

Verilog HDL语言

主讲：李榕

Email: lr@hust.edu.cn

QQ: 179825425

华中科技大学计算机科学与技术学院

Verilog程序设计方法

Module Styles

- Modules can be specified different ways
 - Structural（结构描述） – connect primitives and modules
 - Dataflow（数据流描述） – use continuous assignments
 - Behavioral（行为描述） – use initial and always blocks
- A single module can use more than one method!
- What are the differences?

Structural Example

```
module majority (major, V1, V2, V3) ;
```


```
output major ;  
input V1, V2, V3 ;
```

```
wire N1, N2, N3;
```

```
and A0 (N1, V1, V2),  
      A1 (N2, V2, V3),  
      A2 (N3, V3, V1);
```

```
or Or0 (major, N1, N2, N3);
```

```
endmodule
```

 

Dataflow Example


```
module majority (major, V1, V2, V3) ;
```

```
output major ;
```

```
input V1, V2, V3 ;
```

```
assign major = V1 & V2  
              | V2 & V3  
              | V1 & V3;
```

```
endmodule
```

 

Behavioral Example


```
module majority (major, V1, V2, V3) ;
```

```
output reg major ;
```

```
input V1, V2, V3 ;
```

```
always @(V1, V2, V3) begin  
    if (V1 && V2 || V2 && V3  
        || V1 && V3) major = 1;  
    else major = 0;  
end
```

```
endmodule
```

 

Full Adder: Structural

```
module half_add (X, Y, S, C);  
  
input X, Y ;  
output S, C ;  
  
xor SUM (S, X, Y);  
and CARRY (C, X, Y);  
  
endmodule
```

```
module full_add (A, B, CI, S, CO) ;  
  
input A, B, CI ;  
output S, CO ;  
  
wire S1, C1, C2;  
  
// build full adder from 2 half-adders  
half_add PARTSUM (A, B, S1, C1),  
                SUM (S1, CI, S, C2);  
  
// ... add an OR gate for the carry  
or CARRY (CO, C2, C1);  
  
endmodule
```

Full Adder: RTL/Dataflow

```
module fa_rtl (A, B, CI, S, CO) ;  
  
input A, B, CI ;  
output S, CO ;  
  
// use continuous assignments  
assign S = A ^ B ^ CI;  
assign CO = (A & B) | (A & CI) | (B & CI);  
  
endmodule
```

Data flow Verilog is
often very concise
and still easy to read

Works great for most
boolean and even
datapath descriptions
(最适合组合逻辑设计)

Full Adder: Behavioral


- Circuit “reacts” to given events (for simulation)
 - Actually list of signal changes that affect output

```
module fa_bhv (A, B, CI, S, CO) ;  
  
input A, B, CI;  
output S, CO;  
reg S, CO;           // assignment made in an always block  
                      // must be made to registers  
  
// use procedural assignments  
always@(A or B or CI)  
begin  
    S = A ^ B ^ CI;  
    CO = (A & B) | (A & CI) | (B & CI);  
end  
endmodule
```

Full Adder: Behavioral

- IN SIMULATION
 - When **A**, **B**, or **C** change, **S** and **CO** are recalculated
- IN REALITY
 - Combinational logic – no “waiting” for the trigger
 - *Constantly* computing - think transistors and gates!
 - Same hardware created for all three types of verilog

```
always@(A or B or CI)
begin
    S = A ^ B ^ CI;
    CO = (A & B) | (A & CI) | (B & CI);
end
```

 

Structural Basics: Primitives

- Build design up from the gate/flip-flop/latch level
 - Structural verilog is a netlist of blocks and connectivity
- Verilog provides a set of gate primitives
 - and, nand, or, nor, xor, xnor, not, buf, bufif1, etc.
 - Combinational building blocks for structural design
 - Known “behavior”
 - Cannot access “inside” description
- Can also model at the transistor level
 - Most people don’t, we won’t

Primitives

- No declarations - can only be instantiated
- **Output port appears before input ports**
- Optionally specify: instance name and/or delay (discuss delay later)

and N25 (Z, A, B, C); // name specified

and #10 (Z, A, B, X),

(X, C, D, E); // delay specified, 2 gates

and #10 N30 (Z, A, B); // name and delay specified

Syntax For Structural Verilog


- First declare the interface to the module
 - Module keyword, module name
 - Port names/types/sizes
- Next, declare any internal wires using “wire”
 - wire [3:0] partialsum;
- Then instantiate the primitives/submodules
 - Indicate which signal is on which port
- ModelSim Example with ring oscillator

Hierarchy


- Any Verilog design you do will be a module
- This includes testbenches!
- Interface (“black box” representation)
 - Module name, ports
- Definition
 - Describe functionality of the block
- Instantiation
 - Use the module inside another module

Hierarchy

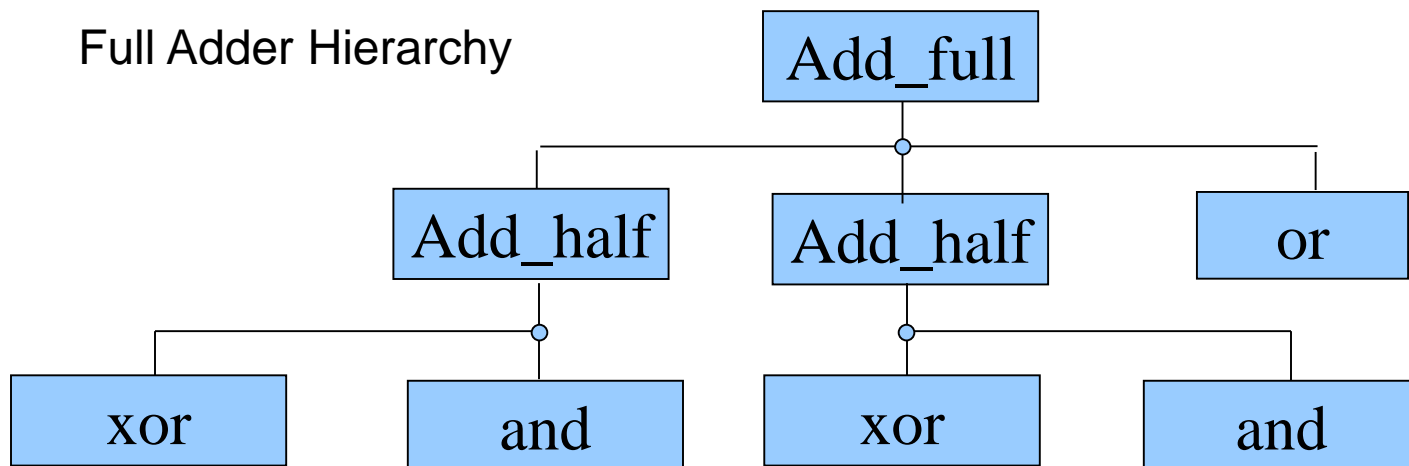- Build up a module from smaller pieces
 - Primitives
 - Other modules (which may contain other modules)
- Design: typically top-down
- Verification: typically bottom-up




Add_half Module

 

```
module Add_half(c_out, sum, a, b);  
  output sum, c_out;  
  input a, b;  
  
  xor sum_bit(sum, a, b);  
  and carry_bit(c_out, a, b);  
endmodule
```


Add_full Module

 

```
module Add_full(c_out, sum, a, b, c_in) ;  
    output sum, c_out;  
    input a, b, c_in;  
    wire w1, w2, w3;  
  
    Add_half AH1(.sum(w1), .c_out(w2), .a(a), .b(b));  
    Add_half AH2(.sum(sum), .c_out(w3), .a(c_in), .b(w1));  
    or carry_bit(c_out, w2, w3);  
endmodule
```

Can Mix Styles In Hierarchy!

```
module Add_half_bhv(c_out, sum, a, b);  
  output reg sum, c_out;  
  input a, b;  
  always @(a, b) begin  
    sum = a ^ b;  
    c_out = a & b;  
  end  
endmodule
```

```
module Add_full_mix(c_out, sum, a, b, c_in) ;  
  output sum, c_out;  
  input a, b, c_in;  
  wire w1, w2, w3;  
  Add_half_bhv AH1(.sum(w1), .c_out(w2),  
                    .a(a), .b(b));  
  Add_half_bhv AH2(.sum(sum), .c_out(w3),  
                    .a(c_in), .b(w1));  
  assign c_out = w2 | w3;  
endmodule
```

Hierarchy And Scope

- Parent cannot access “internal” signals of child
- If you need a signal, must make a port!

Example:

Detecting overflow

Overflow =

cout XOR cout6



Must output

overflow or cout6!

```
module add8bit(cout, sum, a, b);  
    output [7:0] sum;  
    output cout;  
    input [7:0] a, b;  
    wire cout0, cout1,... cout6;  
    FA A0(cout0, sum[0], a[0], b[0], 1'b0);  
    FA A1(cout1, sum[1], a[1], b[1], cout0);  
    ...  
    FA A7(cout, sum[7], a[7], b[7], cout6);  
endmodule
```

Hierarchy And Source Code

  - Can have all modules in a single file
 - Module order doesn't matter!
 - Good for small designs
 - Not so good for bigger ones
 - Not so good for module reuse (cut & paste)
- Can break up modules into multiple files
 - Helps with organization
 - Lets you find a specific module easily
 - Good for module reuse (add file to project)



Structural Verilog: Connections

- Positional or Connect by reference
 - Can be okay in some situations
 - Designs with very few ports
 - Interchangeable input ports (and/or/xor gate inputs)
 - Gets confusing for large #s of ports

```
module dec_2_4_en (A, E_n, D);
```

```
input [1:0] A;  
input E_n;  
output [3:0] D;  
.  
.  
.
```

```
wire [1:0] X;
```

```
wire W_n;
```

```
wire [3:0] word;
```

```
// instantiate decoder
```

```
dec_2_4_en DX (X, W_n, word);
```

Partial code instantiating decoder

Structural Verilog: Connections

- Explicit or Connect by name method
 - Helps avoid “misconnections”
 - Don’t have to remember port order
 - Can be easier to read
 - .<port name>(<signal name>)

```
module dec_2_4_en (A, E_n, D);
```

```
input [1:0] A;
```

```
input E_n;
```

```
output [3:0] D;
```

```
  .  
  .  
  .
```

```
wire [1:0] X;
```

```
wire W_n;
```

```
wire [3:0] word;
```

```
// instantiate decoder
```

```
dec_2_4_en DX
```

```
(.A(X), .E_n(W_n), .D(word));
```

Partial code instatiating decoder

Empty Port Connections

- Example: `module dec_2_4_en(A, E_n, D);`
 - `dec_2_4_en DX (X[1:0], , word);` // E_n is high impedance (z)
 - `dec_2_4_en DX (X[1:0], W_n ,);` // Outputs D[3:0] unused.
- General rules
 - Empty input ports => high impedance state (z)
 - Empty output ports => output not used
- Specify all input ports anyway!
 - Z as an input is very bad...why?
- Helps if no connection to output port name but leave empty:
 - `dec_2_4_en DX(.A(X[3:2]), .E_n(W_n), .D());`

Dataflow Verilog

- The continuous assign statement
 - It is the main construct of Dataflow Verilog
 - It is **deceptively** powerful & useful
- Generic form:

```
assign [drive_strength] [delay] list_of_net_assignments;
```

Where:

list_of_net_assignment ::= net_assignment [{,net_assignment}]

& Where:

Net_assignment ::= net_lvalue = expression

OK...that means just about nothing to me...how about some examples?

Continuous Assign Examples

- Simplest form:

```
// out is a net, a & b are also nets
```

```
assign out = a & b;    // and gate functionality
```

- Using vectors

```
wire [15:0] result, src1, src2;    // 3 16-bit wide vectors
```

```
assign result = src1 ^ src2;    // 16-bit wide XOR
```


- Can you implement a 32-bit adder in a single line?

```
wire [31:0] sum, src1, src2; // 3 32-bit wide vectors
```

```
assign {c_out,sum} = src1 + src2 + c_in; // wow!
```

Back to the Continuous Assign

- More basic generic form:
assign <LHS> = <RHS expression>;
- If RHS result changes, LHS is updated with new value
 - Constantly operating (“continuous”)
 - It’s ***hardware!***
- RHS can use operators (i.e. +,-,&|,^,~,>>,...)

 

assign {c_out,sum} = src1 + src2 + c_in;

Lets Kick up the Horse Power

- You thought a 32-bit adder in one line was powerful. Lets try a 32-bit MAC...

Design a multiply-accumulate (MAC) unit that computes

$$Z[31:0] = A[15:0] * B[15:0] + C[31:0]$$

It sets overflow to one, if the result cannot be represented using 32 bits.

```
module mac(output [31:0] Z, output overflow,  
           input [15:0] A, B, input [31:0] C);
```

Lets Kick up the Horse Power

```
module mac(output [31:0] Z, output overflow,  
           input [15:0] A, B, input [31:0] C);  
    assign {overflow, Z} = A*B + C;  
endmodule
```

I am a brilliant genius. I am a HDL coder extraordinaire. I created a 32-bit MAC, and I did it in a single line.

assign {overflow, Z} = A*B + C;

Oh my god, I've
created a
monster


Synopsys



```

module mac(output [31:0] Z, output overflow,
            input [15:0] A, B, input [31:0] C);
    assign {overflow, Z} = A*B + C;
endmodule

```

 


Utilization - Post-Implementation			
Resource	Utilization	Available	Utilization %
I/O	97	210	46.19
DSP48	1	240	0.42


[Graph](#)
[Table](#)

[Post-Synthesis](#)
[Post-Implementation](#)

98 Cells 97 I/O Ports 197 Nets

 

522 Cells 97 I/O Ports 888 Nets

 

A Few Other Possibilities

- The implicit assign
 - Goes in the wire declaration
wire [3:0] sum = a + b;
 - Can be a useful shortcut to make code succinct, but doesn't allow fancy LHS combos
assign {cout, sum} = a + b + cin;
- Personal choice
 - ✓ You are welcome to use it when appropriate (**I never do!**)

Behavioral Verilog

- **initial** and **always** form basis of all behavioral Verilog
 - All other behavioral statements occur within these
 - **initial** and **always** blocks cannot be nested
 - All <LHS> assignments must be to type **reg**
- **initial** statements start at time 0 and execute once
 - If there are multiple **initial** blocks they all start at time 0 and execute independently. They may finish independently.
- If multiple behavioral statements are needed within the initial statement then the initial statement can be made compound with use of **begin/end**

More on **initial** statements

- Initial statement very useful for testbenches
- Initial statements **don't** synthesize
- Don't use them in DUT (Device Under Test, 被测设备) Verilog (stuff you intend to synthesize)

initial Blocks

```
`timescale 1 ns / 100 fs
module full_adder_tb;
  reg [3:0] stim;
  wire s, c;

  full_adder(sum, carry, stim[2], stim[1], stim[0]); // instantiate DUT

  // monitor statement is special - only needs to be made once,
  initial $monitor(“%t: s=%b c=%b stim=%b”, $time, s, c, stim[2:0]);


  // tell our simulation when to stop
  initial #50 $stop;

  initial begin // stimulus generation
    for (stim = 4'h0; stim < 4'h8; stim = stim + 1) begin
      #5;
    end
  end
endmodule
```

all initial blocks start at time 0

*multi-statement block enclosed by **begin** and **end***

Another **initial** Statement Example

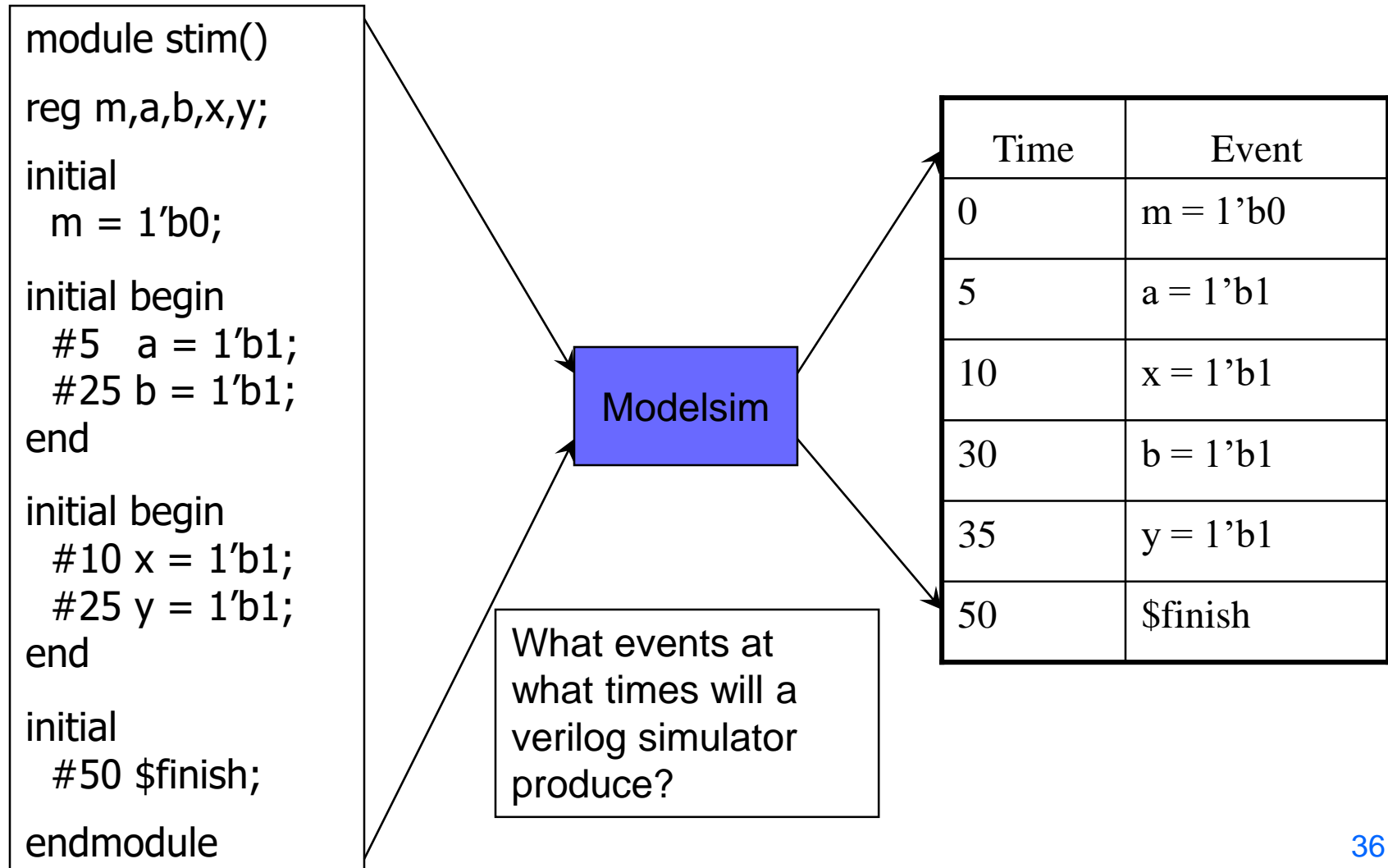

always statements

- Behavioral block operates CONTINUOUSLY
 - Executes at time zero but loops continuously
 - Can use a *trigger list* to control operation; @(a, b, c)
 - In absense of a trigger list it will re-evaluate when the last <LHS> assignment completes.

```
module clock_gen (output reg clock);  
  
  initial  
    clock = 1'b0;           // must initialize in initial block  
  
  always           // no trigger list for this always  
    #10 clock = ~clock;    // always will re-evaluate when  
                           // last <LHS> assignment completes  
  
endmodule
```

always vs initial

```
reg [7:0] v1, v2, v3, v4;
```

```
initial begin
```

```
    v1 = 1;
```

```
    #2 v2 = v1 + 1;
```

```
    v3 = v2 + 1;
```

```
    #2 v4 = v3 + 1;
```

```
    v1 = v4 + 1;
```

```
    #2 v2 = v1 + 1;
```

```
    v3 = v2 + 1;
```

```
end
```

```
reg [7:0] v1, v2, v3, v4;
```

```
always begin
```

```
    v1 = 1;
```

```
    #2 v2 = v1 + 1;
```

```
    v3 = v2 + 1;
```

```
    #2 v4 = v3 + 1;
```

```
    v1 = v4 + 1;
```

```
    #2 v2 = v1 + 1;
```

```
    v3 = v2 + 1;
```

```
end
```

■ What values does each block produce?

➤ Lets take our best guess

➤ Then lets try it in a **simulator**

Trigger lists (Sensitivity lists)

- Conditionally “execute” inside of **always** block
 - Any change on trigger (sensitivity) list, triggers block
- ```
always @(a, b, c) begin
```

...

**end**

- Original way to specify trigger list

```
always @ (X1 or X2 or X3)
```

- In Verilog 2001 can use , instead of **or**

```
always @ (X1, X2, X3)
```

- Verilog 2001 also has \* for *combinational only*

```
always @ (*)
```

Some mixed simulation tools in use today still do not support Verilog 2001.

Do you know your design?

# Example: Comparator

```
module compare_4bit_behave(output reg A_lt_B, A_gt_B, A_eq_B,
 input [3:0] A, B);
```

```
 always@() begin
```

```
 end
```

```
endmodule
```

Flush out this template with sensitivity list and implementation  
**Hint:** a if...else if...else statement is best for implementation



## □ if-else 条件语句

```
if (条件表达式) 块语句1
else if (条件表达式2) 块语句2
.....
else if (条件表达式n) 块语句n
else 块语句n+1
```

## □ case 语句

```
case (敏感表达式)
 值1: 块语句1
 值2: 块语句2

 值n: 块语句n
 default: 块语句n+1
endcase
```

## □ for循环语句

```
for (表达式1; 表达式2; 表达式3) 块语句
```

# if...else if...else statement

- General forms...

```
If (condition) begin
 <statement1>;
 <statement2>;
end
```

Of course the compound statements formed with **begin/end** are optional.

Multiple else if's can be strung along indefinitely


```
If (condition)
begin
 <statement1>;
 <statement2>;
end
else
begin
 <statement3>;
 <statement4>;
end
```

```
If (condition)
begin
 <statement1>;
 <statement2>;
end
else if (condition2)
begin
 <statement3>;
 <statement4>;
end
else
begin
 <statement5>;
 <statement6>;
end
```
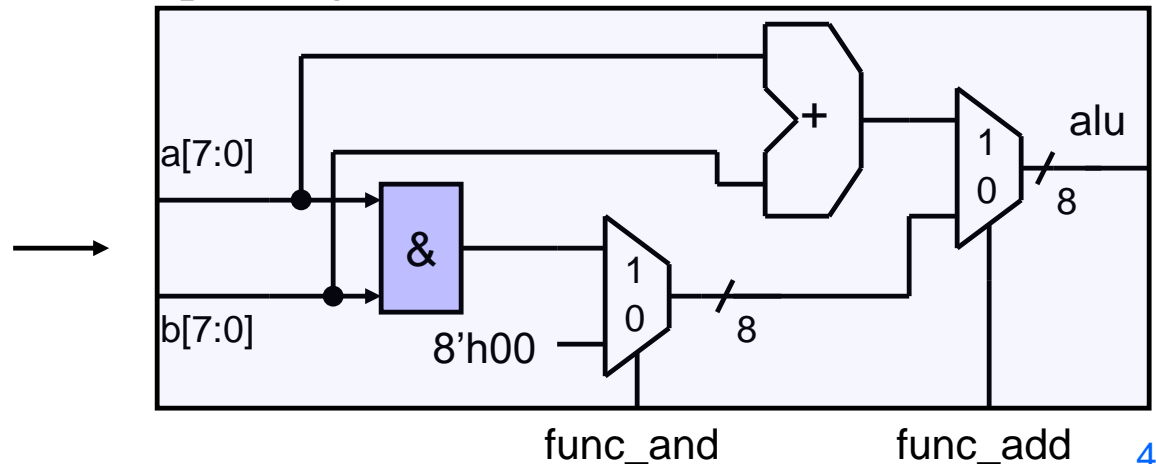
# How does and if...else if...else statement synthesize?

- Does not conditionally “execute” block of “code”
- Does not conditionally create hardware!
- It makes a multiplexer or selecting logic
- Generally:
  - ✓ Hardware for both paths is created
  - ✓ Both paths “compute” simultaneously
  - ✓ The result is selected depending on the condition


```
if (func_add)
 alu = a + b;
else if (func_and)
 alu = a & b;
else
 alu = 8'h00;
```



# if statement synthesis (continued)

```
if (a)
 func = c & d;
else if (b)
 func = c | d;
```

How does this synthesize?

 

What you ask for is what you get!

**func** is of type register. When neither **a** or **b** are asserted it didn't not get a new value.

That means it must have remained the value it was before.

That implies memory...i.e. a **latch**!

Always have an **else** to any **if** to avoid unintended latches.

# More on **if** statements...

- Watch the sensitivity lists...what is missing in this example?

```
always @(a, b) begin
 temp = a - b;
 if ((temp < 8'b0) && abs)
 out = -temp;
 else out = temp;
end
```

```
always @ (posedge clk) begin
 if (reset) q <= 0;
 else if (set) q <= 1;
 else q <= data;
end
```

What is being coded here?

Is it synchronous or asynch?

Does the reset or the set have higher priority?

# case Statements

---

- Verilog has three types of case statements:
  - ⑩ **case**, **casex**, and **casez**
- Performs bitwise match of expression and case item
  - Both must have same bitwidth to match!
- **case**
  - Can detect **x** and **z**! (good for testbenches)
- **casez**
  - Uses **z** and **?** as “don’t care” bits in case items and expression
- **casex**
  - Uses **x**, **z**, and **?** as “don’t care” bits in case items and expression

# Case statement (general form)

```
case (expression)
 alternative1 : statement1; // any of these statements could
 alternative2 : statement2; // be a compound statement using
 alternative3 : statement3; // begin/end
 default : statement4 // always use default for synth stuff
endcase
```

```
parameter AND = 2'b00;
parameter OR = 2'b01;
parameter XOR = 2'b10;

case (alu_op)
 AND : alu = src1 & src2;
 OR : alu = src1 | src2;
 XOR : alu = src1 ^ src2;
 default : alu = src1 + src2;
endcase
```

Why always have a default?

Same reason as always having an else with an if statement.

All cases are specified, therefore no unintended latches.

# Using **case** To Detect **x** And **z**

---

- Only use this functionality in a testbench!
- Example taken from Verilog-2001 standard:

```
case (sig)
 1'bz: $display("Signal is floating.");
 1'bx: $display("Signal is unknown.");
 default: $display("Signal is %b.", sig);
endcase
```



# case Statement

---

- Uses **x**, **z**, and **?** as single-bit wildcards in case item and expression
- Uses first match encountered

```
always @ (code) begin
 case (code) // case expression
 2'b0?: control = 8'b00100110; // case item1
 2'b10: control = 8'b11000010; // case item 2
 2'b11: control = 8'b00111101; // case item 3
 endcase
end
```

- What is the output for code = 2'b01?
- What is the output for code = 2'b1x?

# casez Statement

---

- Uses z, and ? as single-bit wildcards in case item and expression

```
always @ (code) begin
 casez (code)
 2'b0?: control = 8'b00100110; // item 1
 2'bz1: control = 8'b11000010; // item 2
 default: control = 8b'xxxxxxxx; // item 3

 endcase
end
```

- What is the output for code = 2b'01?
- What is the output for code = 2b'zz?

```


if (func_add)
 alu = a + b;
else if (func_and)
 alu = a & b;
else
 alu = 8'h00;

```

```

case({func_add, func_and})
 2'b00: alu = 8'h00;
 2'b01: alu = a & b;
 2'b1x: alu = func_add;
default: alu = 8'h00;
endcase

```

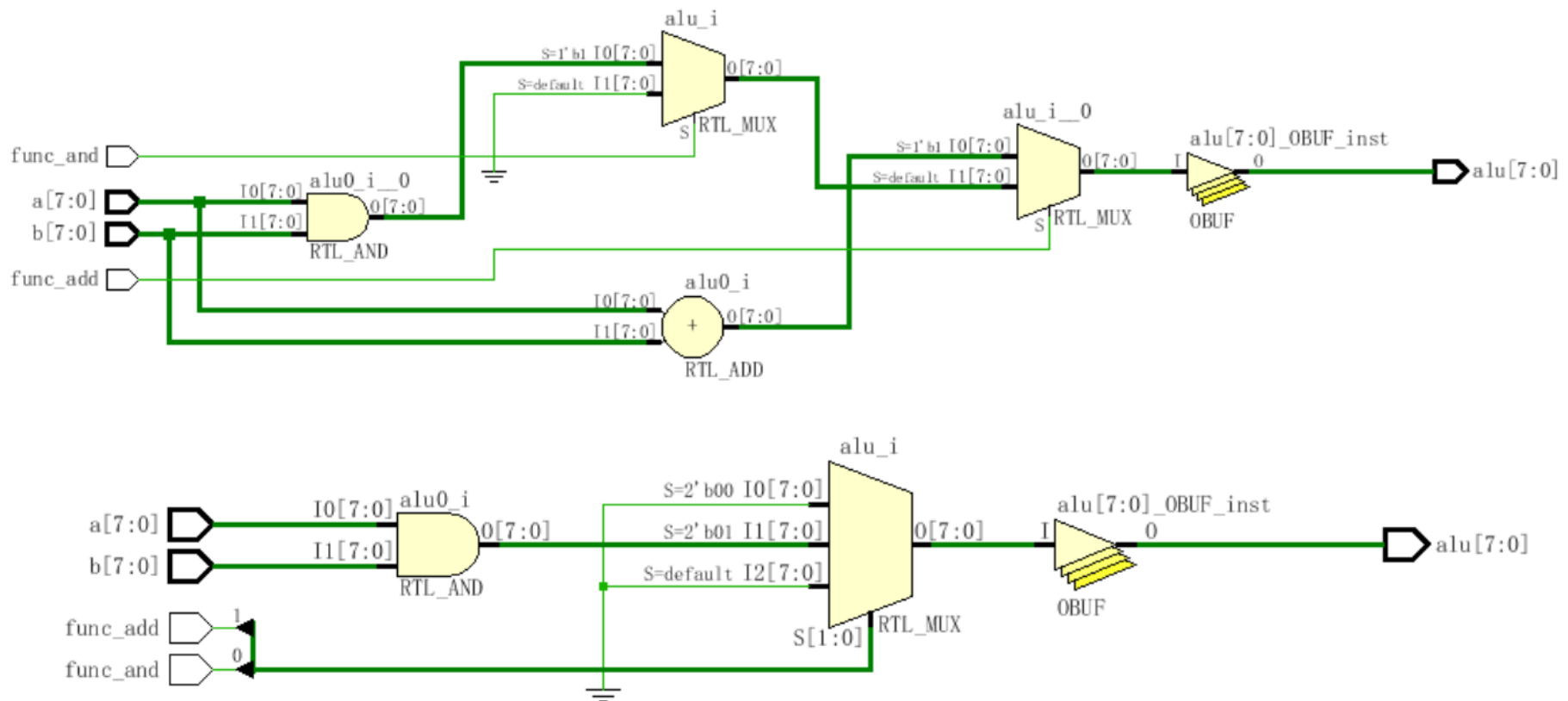

# Loops in Verilog

---

- We already saw the **for** loop:

```
reg [15:0] rf[0:15]; // memory structure for modeling register file
reg [5:0] w_addr; // address to write to

for (w_addr=0; w_addr<16; w_addr=w_addr+1)
 rf[w_addr[3:0]] = 16'h0000; // initialize register file memory
```

- There are 3 other loops available:
  - While loops
  - Repeat loop
  - Forever loop

# while loops

---

- Executes until boolean condition is not true
  - ⑩ If boolean expression false from beginning it will never execute loop

```
reg [15:0] flag;
reg [4:0] index;

initial begin
 index=0;
 found=1'b0;
 while ((index<16) && (!found)) begin
 if (flag[index]) found = 1'b1;
 else index = index + 1;
 end
 if (!found) $display("non-zero flag bit not found!");
 else $display("non-zero flag bit found in position %d",index);
end
```

Handy for cases where  
loop termination is a  
more complex function.

Like a search

# repeat Loop

---

- Good for a fixed number of iterations
  - ⑩ Repeat count can be a variable but...
    - ✓ It is only evaluated when the loops starts
    - ✓ If it changes during loop execution it won't change the number of iterations
- Used in conjunction with @(posedge clk) it forms a handy & succinct way to wait in testbenches for a fixed number of clocks

## **initial begin**

```
inc_DAC = 1'b1;
repeat(4095) @(posedge clk); // bring DAC right up to point of rollover
inc_DAC = 1'b0;
inc_smpl = 1'b1;
repeat(7)@(posedge clk); // bring sample count up to 7
inc_smpl = 1'b0;
```

**end**

# forever loops

---

- We got a glimpse of this already with clock generation in testbenches.
- Only a **\$stop**, **\$finish** or a specific **disable** can end a **forever** loop.

```
initial begin
```

```
 clk = 0;
```

```
 forever #10 clk = ~ clk;
end
```

Clock generator is by far the most common use of a forever loop

```

module mult4b(output reg [7:0] R, input [3:0] A, input [3:0] B);
 integer i;

```

```

 always @(A, B) begin

```

```

 R = 0;

```

```

 for(i=1; i<=4; i=i+1)

```

```

 if(B[i-1]) R = R + (A<<i);

```

```


 end

```

```

 endmodule

```

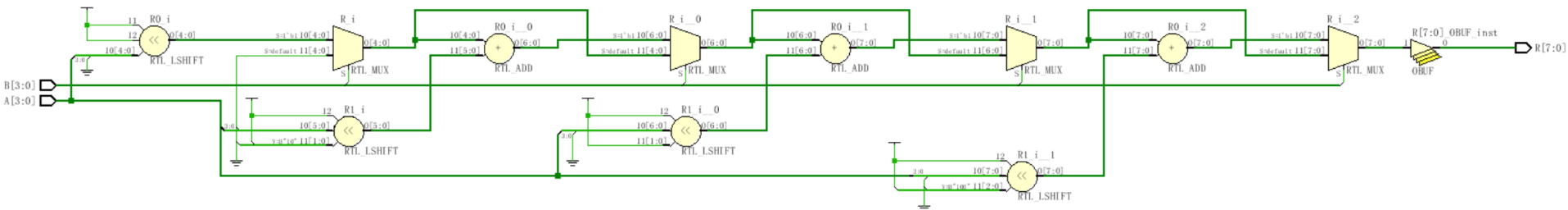



## ❑ 赋值语句

**基本形式：** <寄存器变量>=<表达式>;  
**外部模式：** <定时控制> <寄存器变量>=<表达式>;  
**内部模式：** <寄存器变量>= <定时控制> <表达式>;  
定时控制分为两类： 延时控制  
                                        事件控制 @ (事件控制敏感表)

## ❑ 阻塞型过程赋值

- 赋值算符“=”：前一条语句没有完成赋值过程之前，后面的语句不可能被执行。

## ❑ 非阻塞型过程赋值

- 赋值算符“<=”：一条非阻塞型赋值语句的执行，并不会影响块中其它语句的执行。

## ❑ 连续赋值语句

- 只要输入端操作数的值发生变化，该语句就重新计算并刷新赋值结果。用关键词**assign**来区分。


# Blocking vs non-Blocking

- Blocking “Evaluated” sequentially
- Works a lot like software (**danger!**)
- Used for combinational logic

```
module addtree(output reg [9:0] out,
 input [7:0] in1, in2, in3, in4);

 reg [8:0] part1, part2;
 always @(in1, in2, in3, in4) begin
 part1 = in1 + in2;
 part2 = in3 + in4;
 out = part1 + part2;

 end
endmodule
```

 

# Non-Blocking Assignments

- “Updated” simultaneously if no delays given
- Used for sequential logic

```
module swap(output reg out0, out1, input rst, clk);
```

```
always @(posedge clk) begin
```

```
 if (rst) begin
```

```
 out0 <= 1'b0;
```

```
 out1 <= 1'b1;
```

```
 end
```

```
 else begin
```


```
 out0 <= out1;
```

```
 out1 <= out0;
```

```
 end
```

```
end
```

```
endmodule
```

 


# Swapping if done in Blocking

- In blocking, need a “temp” variable

```
module swap(output reg out0, out1, input in0, in1, swap);

 
reg temp;
always @(*) begin
 out0 = in0;
 out1 = in1;
 if (swap) begin
 temp = out0;
 out0 = out1;
 out1 = temp;
 end
end
endmodule
```



**Which values get included on the sensitivity list from \*?**
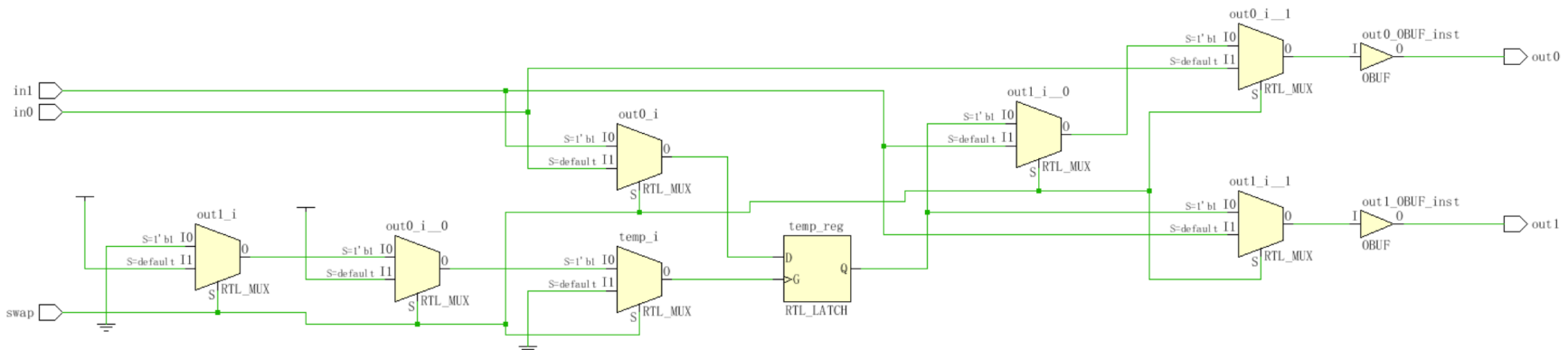
# Swapping if done in Non-Blocking

```
module swap(output reg out0, out1, input in0, in1, swap);
 reg temp;
 always @(*) begin
 out0 <= in0;
 out1 <= in1;
 if (swap) begin
 temp <= out0;
 out0 <= out1;
 out1 <= temp;
 end
 end
endmodule
```




# More on Blocking

- Called blocking because....

⑩ The evaluation of subsequent statements <RHS> are **blocked**, until the <LHS> assignment of the current statement is completed.

```
module pipe(clk, d, q);
input clk,d;
output q;
reg q;

 always @(posedge clk) begin
 q1 = d;
 q2 = q1;
 q3 = q2;
end
endmodule
```



Simulate this in your head...


Remember blocking behavior of:  
<LHS> assigned before  
<RHS> of next evaluated.

Does this work as intended?
 
# More on Non-Blocking

- Lets try that again

```
module pipe(clk, d, q);
input clk,d;
output q;
reg q;
always @(posedge clk) begin
 q1 <= d;
 q2 <= q1;
 q3 <= q2;
End
endmodule;
```



With non-blocking statements the <RHS> of subsequent statements are **not blocked**. They are all evaluated simultaneously.

The assignment to the <LHS> is then scheduled to occur.

This will work as intended.

# So Blocking is no good and we should always use Non-Blocking??

---

- Consider combinational logic

```
module ao4(z,a,b,c,d);
input a,b,c,d;
output z;
reg z,tmp1,tmp2;
always @(a,b,c,d) begin
 tmp1 <= a & b;
 tmp2 <= c & d;
 z <= tmp1 | tmp2;
end
endmodule
```

Does this work?

The inputs (a,b,c,d) in the sensitivity list change, and the always block is evaluated.

New assignments are scheduled for tmp1 & tmp2 variables.

A new assignment is scheduled for z using the **previous** tmp1 & tmp2 values.



# Why not non-Blocking for Combinational

- Can we make this example work?

```
module ao4(z,a,b,c,d);
input a,b,c,d;
output z;
reg z,tmp1,tmp2;
always @(a,b,c,d) begin
 tmp1 <= a & b;
 tmp2 <= c & d;
 z <= tmp1 | tmp2;
end
endmodule
```

Yes

Put tmp1  
& tmp2 in  
the  
trigger  
list

```
module ao4(z,a,b,c,d);
input a,b,c,d;
output z;
reg z,tmp1,tmp2;
always @(a,b,c,d,tmp1,tmp2) begin
 tmp1 <= a & b;
 tmp2 <= c & d;
 z <= tmp1 | tmp2;
end
endmodule
```

What is the downside of this?

❑ 任务（task）

❑ 函数（function）

❑ 任务和函数结构之间的差异：

- 一个任务块可以含有**时间控制结构**，而函数块则没有；
- 一个任务块可以有**输入和输出**，而函数块必须有至少一个输入，没有任何输出；
- 任务块的引发是通过**一条语句**，而函数块只有当它被引用在一个**表达式**中时才会生效。

**task** 任务名；  
端口与类型说明；  
局部变量说明；  
块语句  
**endtask**

**function** <位宽说明> 函数名；  
输入端口与类型说明；  
局部变量说明；  
块语句  
**endfunction**

# functions

---

- Declared and referenced within a module
- Used to implement combinational behavior
  - Contain no timing controls or tasks
- Inputs/outputs
  - Must have at least one input argument
  - Has only one output (no inouts)
  - Function name is implicitly declared return variable
  - Type and range of return value can be specified (1-bit wire is default)

# When to use functions?

---

- Usage rules:
  - ⑩ May be referenced in any expression (RHS)
  - ⑩ May call other functions
- Requirements of procedure (implemented as function)
  - No timing or event control
  - Returns a single value
  - Has at least 1 input
  - Uses only behavioral statements
  - Only uses blocking assignments (combinational)
- Mainly useful for conversions, calculations, and selfchecking routines that return boolean. (testbenches)

# Function Example

```
module word_aligner (word_out, word_in);
 output [7: 0] word_out;
 input [7: 0] word_in;
 assign word_out = aligned_word(word_in); // invoke function

 function [7: 0] aligned_word; // function declaration
 input [7: 0] word;
 begin
 aligned_word = word;
 if (aligned_word != 0)
 while (aligned_word[7] == 0) aligned_word = aligned_word << 1;
 end
 endfunction
endmodule
```

*size of return value*


*input to function*





Does this synthesize?

# Function Example

---

```
23 module word_aligner (word_out, word_in);
24 output [7: 0] word_out;
25 input [7: 0] word_in;
26 assign word_out = aligned_word(word_in); // invoke function
27
28 function [7: 0] aligned_word; // function declaration
29 input [7: 0] word;
30 begin
31 aligned_word = word;
32 if (aligned_word != 0)
33 while (aligned_word[7] == 0) aligned_word = aligned_word << 1;
34 end
35 endfunction
36 endmodule
```

 **Vivado Commands** (3 errors)

-  **synth\_design -rtl -name rtl\_1** (3 errors)
  -  [Synth 8-3380] loop condition does not converge after 2000 iterations [[word\\_aligner.v:33](#)]
  -  [Synth 8-285] failed synthesizing module 'word\_aligner' [[word\\_aligner.v:23](#)]
  -  [Vivado\_Icl 4-5] Elaboration failed - please see the console for details

# Function Example [2]

```
module arithmetic_unit (result_1, result_2, operand_1, operand_2,);
```

```
 output [4: 0] result_1;
```

```
 output [3: 0] result_2;
```

```
 input [3: 0] operand_1, operand_2;
```

```
 assign result_1 = sum_of_operands (operand_1, operand_2);
```

```
 assign result_2 = larger_operand (operand_1, operand_2);
```

*function call*



```
function [4: 0] sum_of_operands(input [3:0] operand_1, operand_2);
```

```
 sum_of_operands = operand_1 + operand_2;
```

```
endfunction
```

*function output*



*function inputs*




```
function [3: 0] larger_operand(input [3:0] operand_1, operand_2);
```

```
 larger_operand = (operand_1 >= operand_2) ? operand_1 : operand_2;
```

```
endfunction
```

```
endmodule
```

# Function Example [2]

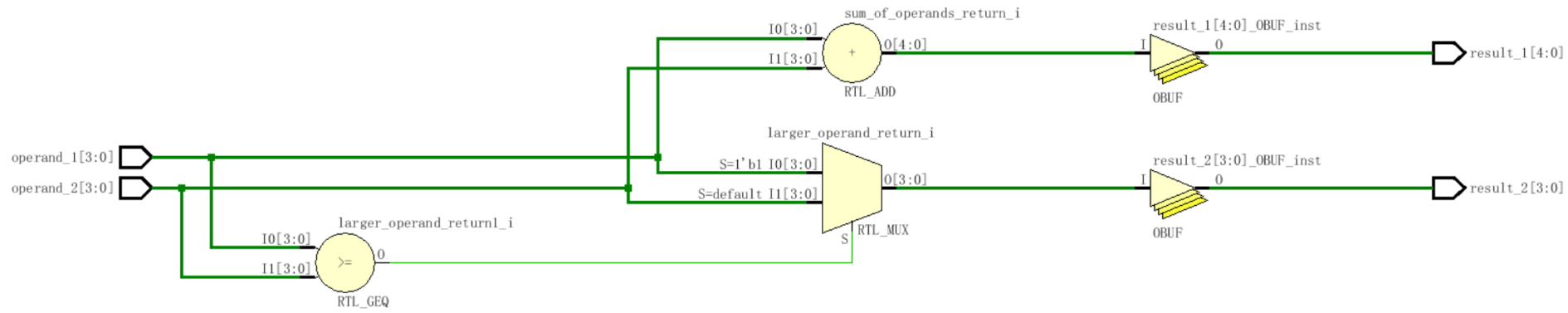



# Re-Entrant (recursive) functions

---

- Use keyword **automatic** to enable stack saving of function working space and enable recursive functions.

```
module top;

//Define the factorial function
function automatic integer factorial;
input [31:0] oper;

begin
 if (oper>=2)
 factorial = factorial(oper-1)*oper;
 else
 factorial = 1;
end

endfunction
```

```
initial begin
 result = factorial(4);
 $display("Result is %d",result);
end

endmodule
```

Is this how you would do it?

KISS

# tasks (much more useful than functions)

| Functions:                                                                         | Tasks:                                                                                          |
|------------------------------------------------------------------------------------|-------------------------------------------------------------------------------------------------|
| A function can enable another function, but not another task                       | A task can enable other tasks and functions                                                     |
| Functions must execute in zero delay                                               | Tasks may execute in non-zero simulation time                                                   |
| Functions can have no timing or even control statements                            | Tasks may contain delay, event or timing control. (i.e. $\rightarrow$ @, #)                     |
| Function must have at least one input argument.                                    | Task may have zero or more arguments of type input, output, or inout                            |
| Functions always return a single value. They cannot have output or inout arguments | Tasks do not return a value, but rather pass multiple values through output and input arguments |

Tasks can modify global signals too, perhaps naughty, but I do it all the time.

# Why use Tasks?


---

- Tasks provide the ability to
  - ⑩ Execute common procedures from multiple places
  - ⑩ Divide large procedures into smaller ones
- Local variables can be declared & used
- Personally, I only use tasks in testbenches, but they are very handy there.
  - Break common testing routines into tasks
    - ✓ Initialization tasks
    - ✓ Stimulus generation tasks
    - ✓ Self Checking tasks
  - Top level test then becomes mainly calls to tasks.
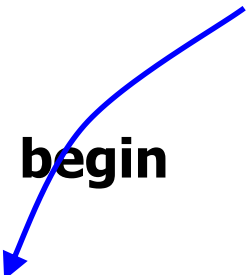
# Task Example [Part 1]

```
module adder_task (c_out, sum, clk, reset, c_in, data_a, data_b);
 output reg [3: 0] sum;
 output reg c_out;
 input [3: 0] data_a, data_b;
 input clk, reset, c_in;

 always @(posedge clk or posedge reset) begin
 if (reset) {c_out, sum} <= 0;
 else add_values (sum, c_out, data_a, data_b, c_in); // invoke task
 end
 // Continued on next slide
```



*Calling of task*

# Task Example [Part 2]

// Continued from previous slide

**task** add\_values;        // task declaration

**output** reg [3: 0] SUM;

**output** reg C\_OUT;

**input** [3: 0] DATA\_A, DATA\_B;

**input** C\_IN;

      {C\_OUT, SUM} = DATA\_A + (DATA\_B + C\_IN);

**endtask**

**endmodule**


} *task outputs*

} *task inputs*

- Could have instead specified inputs/outputs using a port list.

**task** add\_values (**output reg** [3: 0] SUM, **output reg** C\_OUT,  
                  **input** [3:0] DATA\_A, DATA\_B, **input** C\_IN);

# Task Example [Part 3]

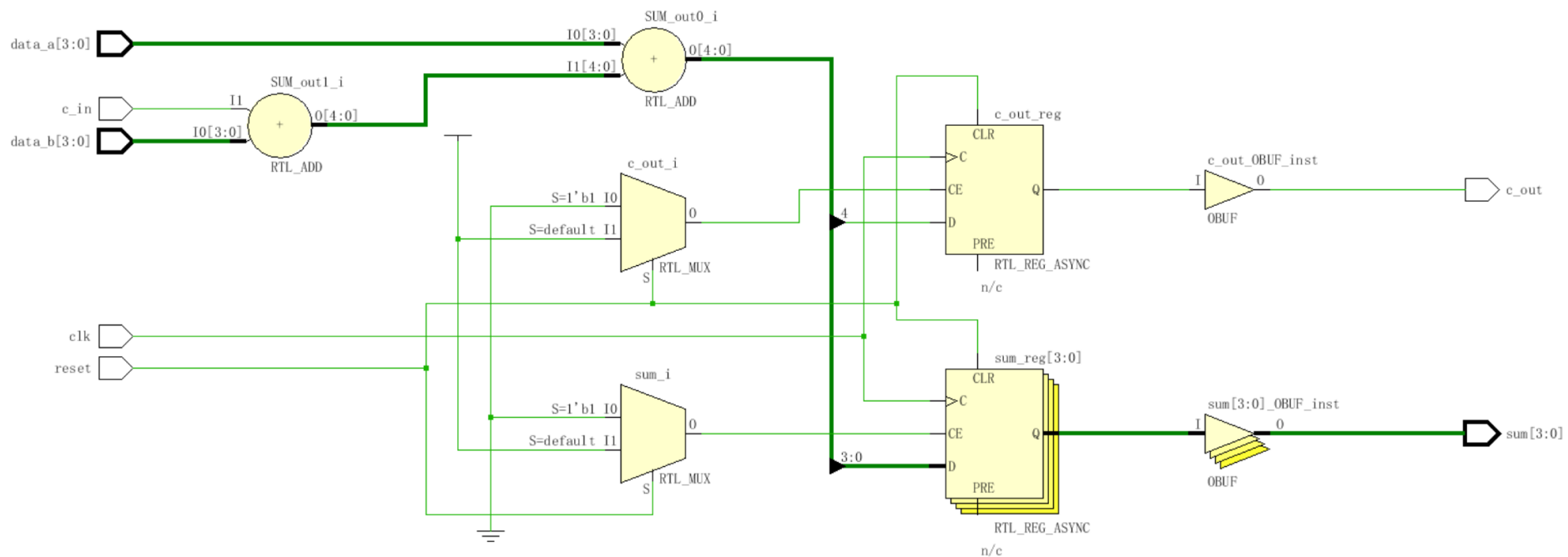

# Task Example [2]

```
task leading_1(output reg [2:0] position, input [7:0]
data_word);
```

```
 reg [7:0] temp;
```

```
 begin
```

```
 temp = data_word;
```

```
 position = 7;
```

```
 while (!temp[7]) begin
```

```
 temp = temp << 1;
```

```
 position = position - 1;
```

```
 end
```

```
 end
```

```
endtask
```

*internal task variable*

**NOTE:**

***"while" loops usually  
not synthesizable!***

- What does this task assume for it to work correctly?
- How do tasks differ from modules?
- How do tasks differ from functions?

## □ 时序控制

- 由“#”符号引入的**延迟控制**。它将程序的执行过程中断一定的时间，时间的长度由<time>的值来确定。

```
<time> <statement> ;
```

- 由“@”符号引入的**事件控制**。一个事件可以通过运行表达式“->event”变量被激发。

```
@ (<posedge>|<negedge>|<signals>) <statement>;
```

- **等待语句**。直到表达式计算为真之前，都延时下一个语句的执行。

```
wait (<expression>) <statement> ;
```

- **延迟定义块**。对模块中某一指定的路径进行延迟定义，这一路径连接模块的输入端口与输出端口（或双向端口）。

```
specify
 (<expression>) = <time>

endspecify
```




# Named Blocks

- Blocks (**begin/end**) or (**fork/join**) can be named
  - Local variables can be declared for the named block
  - Variables in a named block can be accessed using hierarchical naming reference
  - Named blocks can be disabled (i.e. execution stopped)

```
module top();

initial begin: block1
 integer i; // i is local to block1
 // top.block1.i
 ...
end // end of block1

endmodule
```

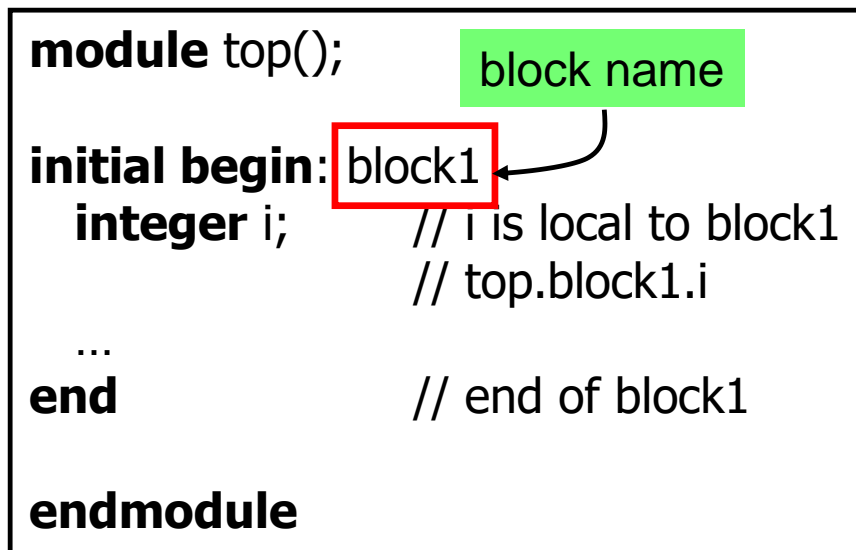

# disable Statement

- Similar to the “break” statement in C
  - Disables execution of the current block (not permanently)

```
begin : break
 for (i = 0; i < n; i = i+1) begin : continue
 @(posedge clk)
 if (a == 0) // "continue" loop
 disable continue;
 if (a == b) // "break" from loop
 disable break;
 statement1
 statement2
 end
end
```

What occurs if (a==0)?

What occurs if (a==b)?

How do they differ?

# File I/O – Why?

- If we don't want to hard-code all information in the testbench, we can use input files
- Help automate testing
  - One file with inputs
  - One file with expected outputs
- Can have a software program generate data
  - Create the inputs for testing
  - Create “correct” output values for testing
  - Can use files to “connect” hardware/software system

# Opening/Closing Files

- **\$fopen** opens a file and returns an integer descriptor
  - integer fd = \$fopen(“filename”);**
  - integer fd = \$fopen(“filename”, r);**
  - If file cannot be open, returns a 0
  - Can output to more than one file simultaneously by writing to the OR ( | ) of the relevant file descriptors
    - ✓ Easier to have “summary” and “detailed” results
- **\$fclose** closes the file
  - \$fclose(fd);**

# Writing To Files

- Output statements have file equivalents
  - ✓ **\$fmonitor()**
  - ✓ **\$fdisplay()**
  - ✓ **\$fstrobe()**
  - ✓ **\$fwrite()**      // write is like a display without the \n
- These system calls take the file descriptor as the first argument
  - ✓ **\$fdisplay(fd, "out=%b in=%b", out, in);**

# Reading From Files

- Read a binary file: `$fread(destination, fd);`
  - Can specify start address & number of locations too
  - Good luck! I have never used this.
- Very rich file manipulation (see IEEE Standard)
  - ✓ `$fseek()`, `$fflush()`, `$ftell()`, `$rewind()`, ...
- Will cover a few of the more common read commands next

# Using **\$fgetc** to read characters

```
module file_read()
parameter EOF = -1;
integer file_handle,error,indx;
reg signed [15:0] wide_char;
reg [7:0] mem[0:255];
reg [639:0] err_str;

initial begin
 indx=0;
 file_handle = $fopen("text.txt","r");
 error = $ferror(file_handle,err_str);
 if (error==0) begin
 wide_char = 16'h0000;
 while (wide_char!=EOF) begin
 wide_char = $fgetc(file_handle);
 mem[indx] = wide_char[7:0];
 $write("%c",mem[indx]);
```

```
 indx = indx + 1;
 end
 end
 else $display("Can't open file...");
 $fclose(file_handle);
end
endmodule
```

The quick brown fox jumped  
over the lazy dogs

*text.txt*

When finished the array *mem* will contain the characters of this file one by one, and the file will have been echoed to the screen.

Why wide\_char[15:0] and why signed?

# Using **\$fgets** to read lines

```
module file_read2()

integer file_handle,error,indx,num_bytes_in_line;
reg [256*8:1] mem[0:255],line_buffer;
reg [639:0] err_str;

initial begin
 indx=0;
 file_handle = $fopen("text2.txt","r");
 error = $ferror(file_handle,err_str);
 if (error==0) begin
 num_bytes_in_line = $fgets(line_buffer,file_handle);
 while (num_bytes_in_line>0) begin
 mem[indx] = line_buffer;
 $write("%s",mem[indx]);
 indx = indx + 1;
 num_bytes_in_line = $fgets(line_buffer,file_handle);
 end
 end
 else $display("Could not open file text2.txt");
```

**\$fgets()** returns the number of bytes in the line. When this is a zero you know you hit EOF.



# Using **\$fscanf** to read files

```
module file_read3()
integer file_handle,error,indx,num_matches;
reg [15:0] mem[0:255][1:0];
reg [639:0] err_str;

initial begin
 indx=0;
 file_handle = $fopen("text3.txt","r");
 error = $ferror(file_handle,err_str);
 if (error==0) begin
 num_matches = $fscanf(file_handle,"%h %h",mem[indx][0],mem[indx][1]);
 while (num_matches>0) begin
 $display("data is: %h %h",mem[indx][0],mem[indx][1]);
 indx = indx + 1;
 num_matches = $fscanf(file_handle,"%h %h",mem[indx][0],mem[indx][1]);
 end
 end
 else $display("Could not open file text3.txt");
```

|      |      |
|------|------|
| 12f3 | 13f3 |
| abcd | 1234 |
| 3214 | 21ab |

|                  |
|------------------|
| <i>text3.txt</i> |
|------------------|

# Loading Memory Data From Files

- This is very useful (memory modeling & testbenches)
  - \$readmemb("<file\_name>",<memory>);
  - \$readmemb("<file\_name>",<memory>,<start\_addr>,<finish\_addr>);
  - \$readmemh("<file\_name>",<memory>);
  - \$readmemh("<file\_name>",<memory>,<start\_addr>,<finish\_addr>);
- **\$readmemh** → Hex data...**\$readmemb** → binary data
  - But they are reading ASCII files either way (just how numbers are represented)

| // addr | data     |
|---------|----------|
| @0000   | 10100010 |
| @0001   | 10111001 |
| @0002   | 00100011 |

example "binary" file

| // addr | data |
|---------|------|
| @0000   | A2   |
| @0001   | B9   |
| @0002   | 23   |

example "hex" file

| //data |
|--------|
| A2     |
| B9     |
| 23     |

address is optional for the lazy

# Example of \$readmemh

```
module rom(input clk; input [7:0] addr; output [15:0] dout);

reg [15:0] mem[0:255]; // 16-bit wide 256 entry ROM
reg [15:0] dout;

initial
 $readmemh("constants",mem);

always @(negedge clk) begin
 //////////////////////////////////////
 // ROM presents data on clock low //
 //////////////////////////////////////
 dout <= mem[addr];
end

endmodule
```

# 'Include Compiler Directives

- **`include** filename
  - Inserts entire contents of another file at compilation
  - Can be placed anywhere in Verilog source
  - Can provide either relative or absolute path names
- Example 1:

```
module use_adder8(...);
 `include "adder8.v" // include the task for adder8
```
- Example 2:

```
module cppc_dig_tb();
 `include "/home/ehoffman/ece551/project/tb_tasks.v"
```
- Useful for including tasks and functions in multiple modules