

Verilog HDL语言

主讲：李榕

Email: lr@hust.edu.cn

QQ: 179825425

华中科技大学计算机科学与技术学院

Verilog组合电路设计

- ❑ 运算器
- ❑ 编码器（带优先级）
- ❑ 译码器
- ❑ 数据选择器
- ❑ 数据分配器
- ❑ 数值比较器

// 1位全加器

module fa_rtl (A, B, CI, S, CO) ;

input A, B, CI ;

output S, CO ;

// use continuous assignments

assign S = A ^ B ^ CI;

assign CO = (A & B) | (A & CI) | (B & CI);

endmodule

// 1位全加器

module fa_bhv (A, B, CI, S, CO) ;

input A, B, CI;

output S, CO;

reg S, CO; // assignment made in an always block
 // must be made to registers

// use procedural assignments

always@(A or B or CI)

begin

S = A ^ B ^ CI;


CO = (A & B) | (A & CI) | (B & CI);

end

endmodule

// 1位全加器
 
```
module Add_full(c_out, sum, a, b, c_in) ;  
    output sum, c_out;  
    input a, b, c_in;  
    wire w1, w2, w3;  
  
    Add_half AH1(.sum(w1), .c_out(w2), .a(a), .b(b));  
    Add_half AH2(.sum(sum), .c_out(w3), .a(c_in), .b(w1));  
    or carry_bit(c_out, w2, w3);  
endmodule
```



// 4位全加器


```
module full_adder(a, b, c, s);  
    input  [3:0]  a, b;  
    output [3:0]  s;  
    output        c;  
  
    assign {c,s} = a + b;  
  
endmodule
```

// 多位全加器

```
module full_adder(a, b, c, s);  
    parameter WIDTH = 8;  
  
    input  [WIDTH-1:0]    a, b;  
    output [WIDTH-1:0]    s;  
    output                c;  
  
    assign {c,s} = a + b;  
  
endmodule
```


- ❑ **优先级编码器：** 常用于中断的优先级控制。例如，74LS148是一个8输入，3位二进制码输出的优先级编码器，当其某一个输入有效时，就可以输出一个对应的3位二进制编码。另外，当同时有几个输入有效时，将输出优先级最高的那个输入所对应的二进制编码。

输 入								二进制编码输出		
input(7)	input(6)	input(5)	input(4)	input(3)	input(2)	input(1)	input(0)	y2	y1	y0
X	X	X	X	X	X	X	0	1	1	1
X	X	X	X	X	X	0	1	1	1	0
X	X	X	X	X	0	1	1	1	0	1
X	X	X	X	0	1	1	1	1	0	0
X	X	X	0	1	1	1	1	0	1	1
X	X	0	1	1	1	1	1	0	1	0
X	0	1	1	1	1	1	1	0	0	1
X	1	1	1	1	1	1	1	0	0	0

 

```

module Priority_Encoder(in, y);
    input    [7:0]    in;
    output reg [2:0]    y;

    always @(in) begin
        if(in[0]==1'b0)            y = 3'b111;
        else if(in[1]==1'b0)       y = 3'b110;
        else if(in[2]==1'b0)       y = 3'b101;
        else if(in[3]==1'b0)       y = 3'b100;
        else if(in[4]==1'b0)       y = 3'b011;
        else if(in[5]==1'b0)       y = 3'b010;
        else if(in[6]==1'b0)       y = 3'b001;
        else                        y = 3'b000;
    end
endmodule

```

❑ **3-8译码器：**3-8译码器是最常用的一种小规模集成电路。对输入a、b、c的值进行译码，就可以确定输出端y0~y7的哪一个输出端变为有效，从而达到译码的目的。

选 通 输 入			二进制输入端			译 码 输 出 端							
g1	g2a	g2b	c	b	a	y0	y1	y2	y3	y4	y5	y6	y7
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	1	X	X	X	1	1	1	1	1	1	1	1
0	X	X	X	X	X	1	1	1	1	1	1	1	1
1	0	0	0	0	0	0	1	1	1	1	1	1	1
1	0	0	0	0	1	1	0	1	1	1	1	1	1
1	0	0	0	1	0	1	1	0	1	1	1	1	1
1	0	0	0	1	1	1	1	1	0	1	1	1	1
1	0	0	1	0	0	1	1	1	1	0	1	1	1
1	0	0	1	0	1	1	1	1	1	1	0	1	1
1	0	0	1	1	0	1	1	1	1	1	1	0	1
1	0	0	1	1	1	1	1	1	1	1	1	1	0




```

module decoder_38(out,in,g1,g2a,g2b);
    output reg [7:0] out;
    input      [2:0] in;
    input      g1,g2a,g2b;
    always @(in,g1,g2a,g2b) begin
        if(g1==1'b1 && g2a==1'b0 && g2b==1'b0)
            case(in)
                3'd0: out=8'b11111110;
                3'd1: out=8'b11111101;
                3'd2: out=8'b11111011;
                3'd3: out=8'b11110111;
                3'd4: out=8'b11101111;
                3'd5: out=8'b11011111;
                3'd6: out=8'b10111111;
                3'd7: out=8'b01111111;
            endcase
        end
    end
endmodule

```


❑ 1位数据宽度2选1多路选择器

 

```
module mux2_1(out1, a, b, sel) ;  
    output reg out1;  
    input a, b;  
    input sel;  
always @(sel or a or b)  
begin  
    if (sel)  
        out1 = b;  
    else  
        out1 = a;  
end  
endmodule
```

```
module mux2_1(out1, a, b, sel) ;  
    output reg out1;  
    input a, b;  
    input sel;  
always @(sel or a or b)  
begin  
    case (sel)  
        1'b0 : out1 = a;  
        1'b1 : out1 = b;  
    endcase  
end  
endmodule
```

❑ 多位数据宽度2选1多路选择器

 

```
module mux2_1(out1, a, b, sel) ;  
    output reg [3:0] out1;  
    input      [3:0] a, b;  
    input      sel;  
always @(sel or a or b)  
begin  
    if (sel)  
        out1 = b;  
    else  
        out1 = a;  
end  
endmodule
```

```
module mux2_1(out1, a, b, sel) ;  
    output reg [3:0] out1;  
    input      [3:0] a, b;  
    input      sel;  
always @(sel or a or b)  
begin  
    case (sel)  
        1'b0 : out1 = a;  
        1'b1 : out1 = b;  
    endcase  
end  
endmodule
```

❑ 4选1多路选择器（用if-else 语句描述）

```
module MUX4_1(out, in0, in1, in2, in3, sel);  
    output out;  
    input in0, in1, in2, in3;  
    input[1:0] sel;  
    reg out;  
  
    always @ (in0 or in1 or in2 or in3 or sel)  
    begin  
        if (sel==2'b00)      out=in0;  
        else if (sel==2'b01) out=in1;  
        else if (sel==2'b10) out=in2;  
        else                  out=in3;  
    end  
endmodule
```

❑ 4选1多路选择器（用case 语句描述）

```
module MUX4_1(out, in0, in1, in2, in3, sel);  
    output out;  
    input in0,in1,in2,in3;  
    input[1:0] sel;  
    reg out;  
  
    always @ (in0 or in1 or in2 or in3 or sel)  
    begin  
        case(sel)  
            2'b00: out=in0;  
            2'b01: out=in1;  
            2'b10: out=in2;  
            default: out=in3;  
        endcase  
    end  
endmodule
```


// 数值比较器

```
module comparator(A, B, is_equal, is_great, is_less);  
  parameter WIDTH = 8;  
  input [WIDTH-1:0] A, B;  
  output is_equal, is_great, is_less;  
  
  assign is_equal = (A==B)? 1'b1 : 1'b0;  
  assign is_great = (A>B)? 1'b1 : 1'b0;  
  assign is_less  = (A<B)? 1'b1 : 1'b0;  
endmodule
```

Verilog时序电路设计

❑ 触发器（锁存器）

❑ 寄存器

❑ 计数器

❑ 存储器

■ 基本D触发器及其Verilog表述

 


图 5-1 边沿触发型 D 触发器

 


图 5-2 D 触发器时序波形

【例 5-1】

```
module DFF1(CLK,D,Q);  
    output Q;  
    input CLK,D;  
    reg Q;  
    always @(posedge CLK)  
        Q <= D;  
Endmodule
```

■ 含异步复位和时钟使能的D触发器及其Verilog表述

 


图 5-4 含使能和复位控制的 D 触发器

 


图 5-5 图 5-4 的 D 触发器的时序图

【例 5-4】

```
module DFF2 (CLK, D, Q, RST, EN);  
    output Q;  
    input CLK, D, RST, EN;  
    reg Q;  
    always @(posedge CLK or negedge RST)  
    begin  
        if (!RST) Q <= 0;  
        else if (EN) Q <= D;  
    end  
endmodule
```

■ 含同步复位控制的D触发器及其Verilog表述

 


图 5-6 含同步清 0 控制的 D 触发器

 


图 5-7 含同步清 0 控制 D 触发器的时序图

【例 5-5】

```
module DFF3 (CLK, D, Q, RST);  
    output Q;  
    input CLK, D, RST;  
    reg Q;  
    always @(posedge CLK)  
        if (RST==1) Q = 0;  
        else if (RST==0) Q = D;  
endmodule
```

【例 5-6】

```
module DFF1 (CLK, D, Q, RST);  
    output Q; input CLK, D, RST;  
    reg Q, Q1; //注意定义了 Q1 信号  
    always @(RST) //纯组合过程  
        if (RST==1) Q1=0; else Q1=D;  
    always @(posedge CLK)  
        Q <= Q1;  
endmodule
```

■ 基本锁存器及其Verilog表述

 


图 5-8 锁存器模块

 


图 5-9 锁存器模块内部逻辑电路

【例 5-8】

```
module LATCH1 (CLK, D, Q);  
    output Q ; input CLK, D;  
    reg Q;  
    always @(D or CLK)  
        if (CLK) Q <= D;  
endmodule
```

 


图 5-10 例 5-8 锁存器的时序波形

■ 含清0控制的锁存器及其Verilog表述

 


图 5-11 含异步清 0 的锁存器

 


图 5-12 含异步清 0 锁存器的逻辑电路图

【例 5-9】

```
module LATCH2 (CLK,D,Q,RST);  
    output Q ;    input CLK,D,RST;  
    assign Q = (!RST)? 0:(CLK ? D:Q);  
endmodule
```

 


图 5-13 含异步清 0 的锁存器的仿真波形

【例 5-10】

```
module LATCH3 (CLK,D,Q,RST);  
    output Q ;  
    input CLK,D,RST;  
    reg Q;  
    always @(D or CLK or RST)  
        if(!RST) Q<=0;  
        else if(CLK) Q<=D;  
endmodule
```


■ 异步时序电路的Verilog表述特点

【例 5-11】

```
module AMOD(D,A,CLK,Q);  
    output Q ;    input A,D,CLK;  
    reg Q,Q1;  
    always @(posedge CLK)    Q1 = ~(A|Q) ;  
    always @(posedge Q1)    Q = D;  
endmodule
```

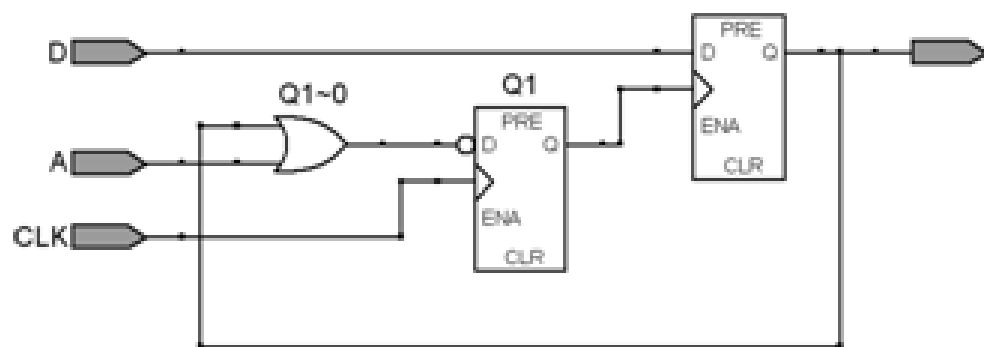


图 5-14 例 5-11 的时序电路图

■ 简单加法计数器及其Verilog表述

 


图 5-16 4 位加法计数器工作时序

 


图 5-17 4 位加法计数器 RTL 电路图

【例 5-13】

```
module CNT4(CLK,Q);  
    output [3:0] Q;    input  CLK;  
    reg [3:0] Q1 ;  
    always @(posedge CLK)  
        Q1 <= Q1+1 ;  
    assign Q=Q1;  
endmodule
```

【例 5-14】

```
module CNT4 (CLK,Q);  
    output [3:0] Q ;  
    input  CLK;  
    reg [3:0] Q ;  
    always @(posedge CLK)  
        Q <= Q+1 ;  
endmodule
```

■ 实用加法计数器

 


图 5-18 例 5-15 的仿真波形图

```

module CNT10 (CLK,RST,EN,LOAD,COUT,DOUT,DATA);
    input CLK,EN,RST,LOAD ;           // 时钟, 时钟使能, 复位, 数据加载控制信号;
    input [3:0] DATA ;               // 4 位并行加载数据
    output [3:0] DOUT ;               // 4 位计数输出
    output COUT ;                     // 计数进位输出
    reg [3:0] Q1 ;    reg COUT ;
    assign DOUT = Q1;                 // 将内部寄存器的计数结果输出至 DOUT
    always @(posedge CLK or negedge RST) //时序过程
    begin
        if (!RST) Q1 <= 0;           //RST=0 时, 对内部寄存器单元异步清 0
        else if (EN) begin            //同步使能 EN=1, 则允许加载或计数
            if (!LOAD) Q1<=DATA;      //当 LOAD=0, 向内部寄存器加载数据
            else if (Q1<9) Q1 <= Q1+1; //当 Q1 小于 9 时, 允许累加
            else Q1 <= 4'b0000; end    //否则一个时钟后清 0 返回初值
        end
    end
    always @(Q1)                      //组合过程
        if (Q1==4'h9) COUT = 1'b1; else COUT = 1'b0;
endmodule

```

■ 含同步预置功能的移位寄存器

【例 5-16】

```
module SHFT1 (CLK, LOAD, DIN, QB) ;  
    output QB;  input CLK, LOAD;  input[7:0] DIN;  reg[7:0] REG8;  
    always @(posedge CLK )  
        if (LOAD)    REG8<=DIN ;  else REG8[6:0]<=REG8[7:1];  
    assign QB = REG8[0] ;  
endmodule
```

 


图 5-20 例 5-16 的工作时序图

■ 使用移位操作符设计移位寄存器

【例 5-17】

```
module SHIF4 (DIN,CLK,RST,DOUT);  
    input CLK,DIN,RST;    output DOUT;    reg [3:0] SHFT;  
    always@(posedge CLK or posedge RST)  
        if(RST)    SHFT<=4'B0;  
        else begin    SHFT <=(SHFT >> 1);    SHFT[3] <= DIN; end  
    assign    DOUT    = SHFT[0];  
endmodule
```

```

// 双端口存储器
module dual_port_ram
#(parameter DATA_WIDTH=8, parameter ADDR_WIDTH=6)(
    input [(DATA_WIDTH-1):0] data,
    input [(ADDR_WIDTH-1):0] read_addr, write_addr,
    input we, clk,
    output reg [(DATA_WIDTH-1):0] q);

    // Declare the RAM variable
    reg [DATA_WIDTH-1:0] ram[2**ADDR_WIDTH-1:0];

    initial begin
        $readmemh("ram_init.txt", ram);    end


    always @ (posedge clk) begin
        // Write
        if (we)    ram[write_addr] <= data;
        q <= ram[read_addr];
    end
endmodule

```

同步时序电路之数据通路


Only Two Types of Circuits Exist

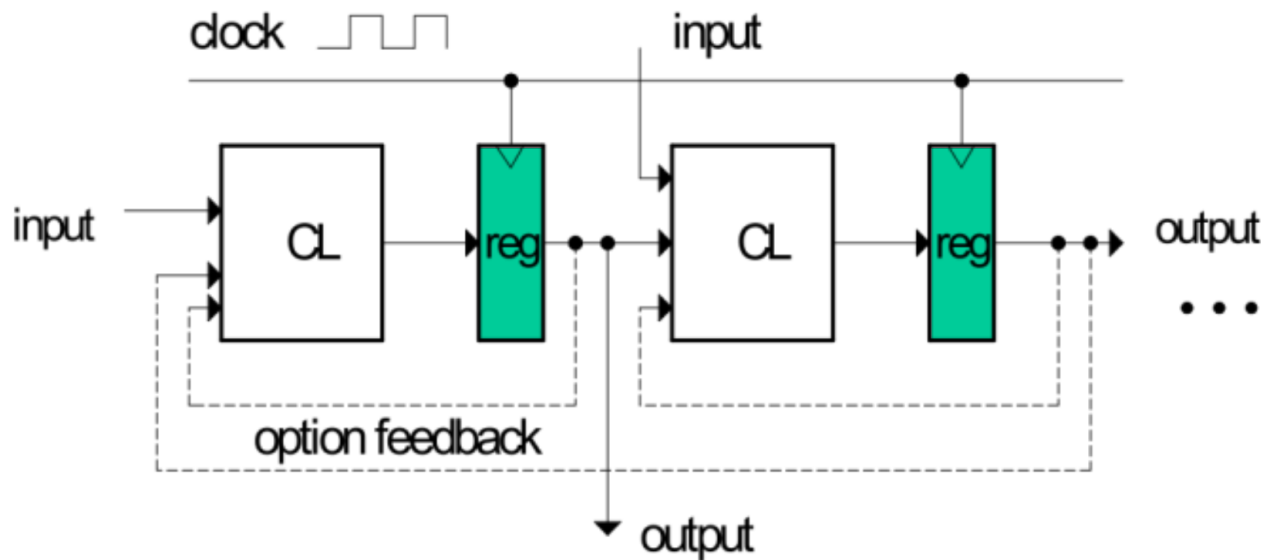- Combinational Logic Blocks (CL) $\leftarrow \text{out} = f(\text{inputs})$
- State Elements (registers) $\leftarrow y_{n+1} = f(\text{inputs}, y_n)$





- State elements are mixed in with CL blocks to control the flow of data.


One Standard High-level Template

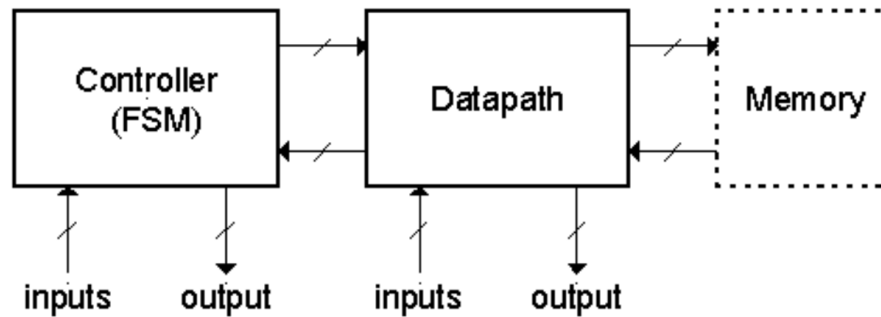

- Controller
 - accepts external and control input, generates control and external output and sequences the movement of data in the datapath. (puppeteer)
 - Datapath
 - is responsible for data manipulation. Usually includes a limited amount of storage. (puppet)
 - Memory
 - optional block used for long term storage of data structures.
- Standard model for CPUs, micro-controllers, many other digital sub-systems.
 - Usually *not* nested.
 - Sometimes cascaded:

 

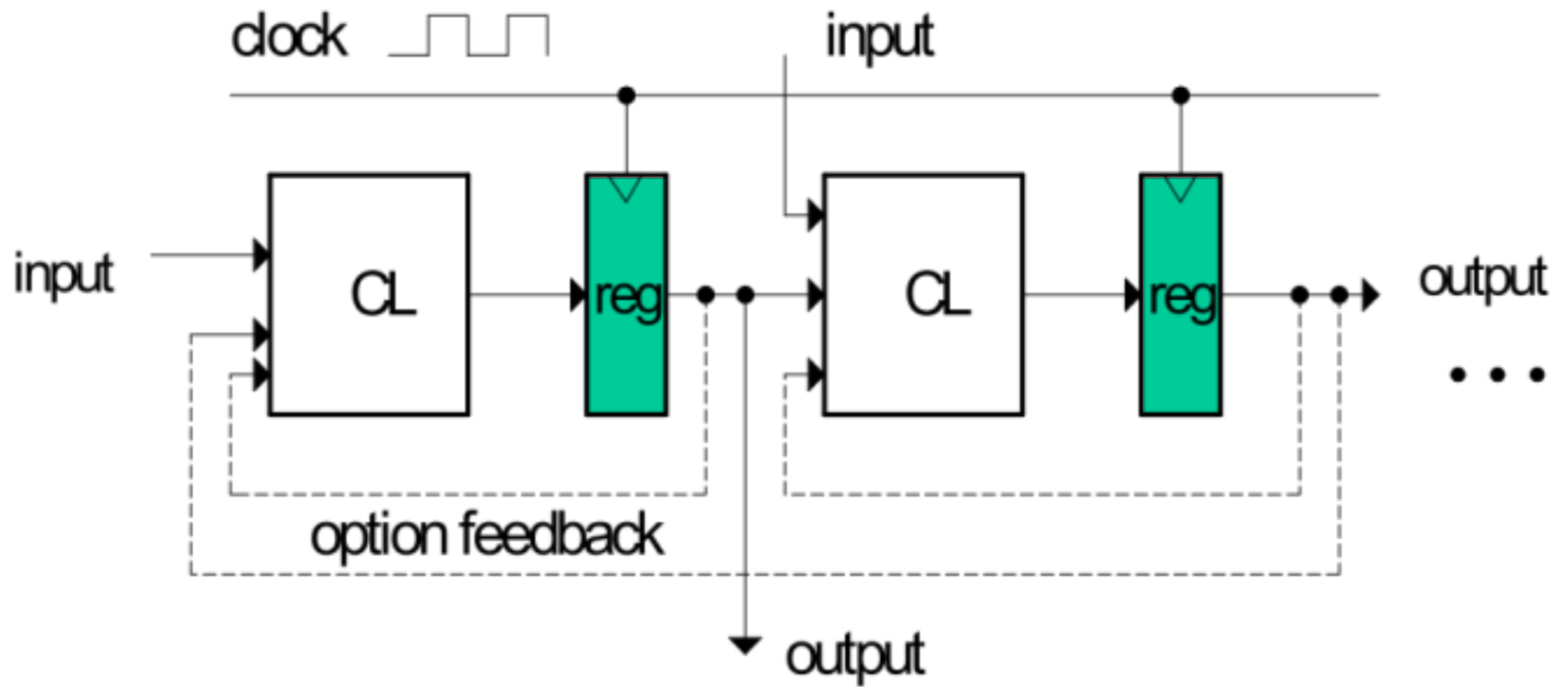

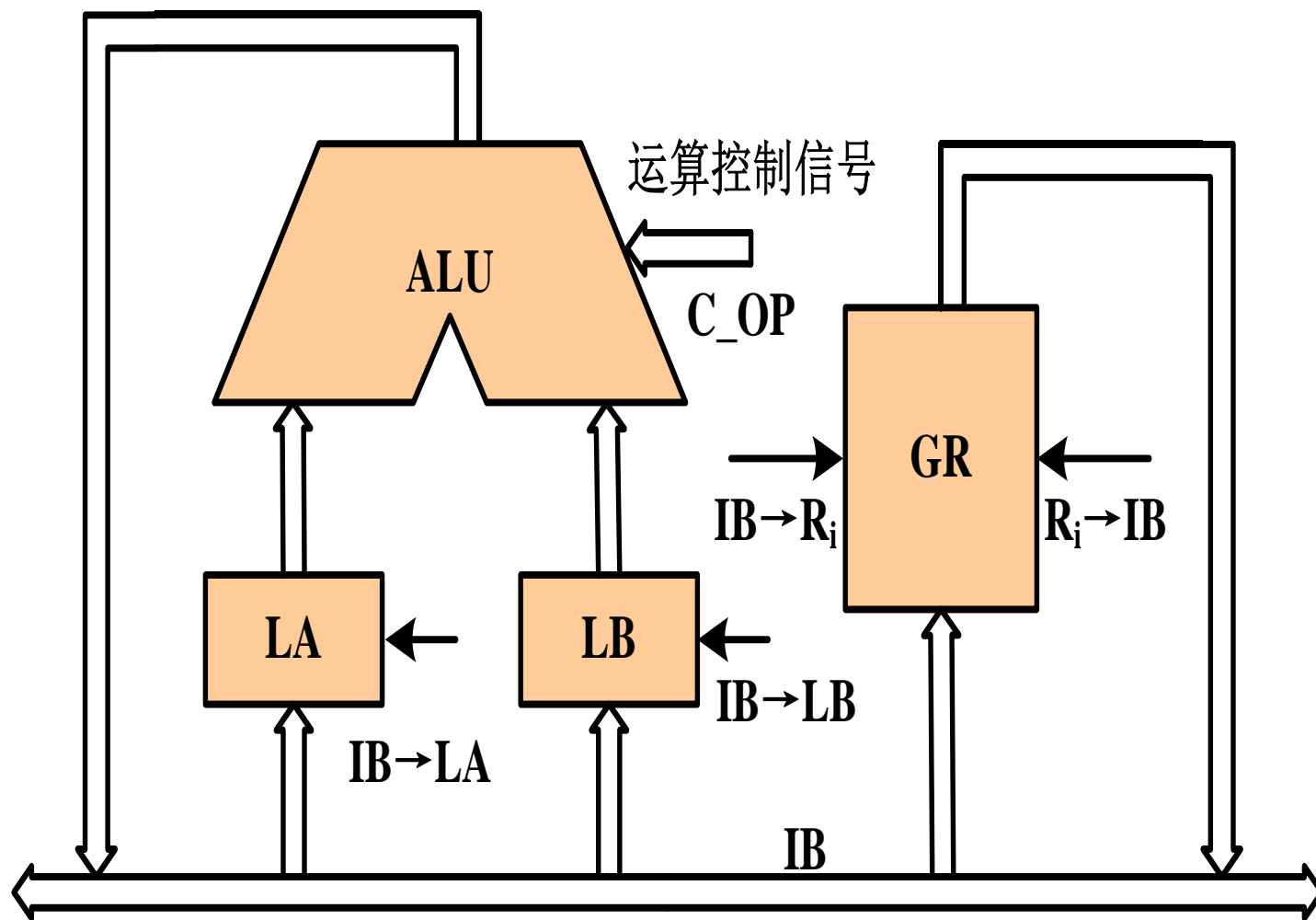

```

} module latch_circuit(clk, rst, ld, d, q);
    parameter WIDTH = 8;
    input clk, rst, ld;
    input [WIDTH-1:0] d;
    output reg [WIDTH-1:0] q;

    always @(posedge clk) begin
        if(rst) q <= 0;
        else if(ld) q <= d;
    end
} endmodule

```

```

module alu_circuit(a, b, op, result);
    parameter WIDTH = 8;
    input [WIDTH-1:0] a, b;
    input [1:0] op;
    output reg [WIDTH-1:0] result;

    always @* begin
        case(op)
            2'b00: result = a + b;
            2'b01: result = a & b;
            2'b10: result = a ^ b;
            2'b11: result = a | b;
            default: result = 0;
        endcase
    end
endmodule

```

```

module register_file
#(parameter DATA_WIDTH=8, parameter ADDR_WIDTH=3)
(
    input [(DATA_WIDTH-1):0] data,
    input [(ADDR_WIDTH-1):0] read_addr, write_addr,
    input we, clk,
    output reg [(DATA_WIDTH-1):0] q
);

    // Declare the RAM variable
    reg [DATA_WIDTH-1:0] ram[2**ADDR_WIDTH-1:0];

    always @ (posedge clk)
    begin
        // Write
        if (we)
            ram[write_addr] <= data;

        q <= ram[read_addr];
    end
endmodule

```


```

module datapath_top(input clk, rst);
    wire [31:0] la_data, lb_data, alu_data, rf_data;
    wire lda, ldb, we;
    wire [4:0] read_addr, write_addr;
    wire [1:0] op;

    latch_circuit #(32) LA (clk, rst, lda, rf_data, la_data);
    latch_circuit #(32) LB (clk, rst, ldb, rf_data, lb_data);
    register_file #(32, 5) GR (alu_data, read_addr, write_addr, we, clk, rf_data);
    alu_circuit #(32) ALU (la_data, lb_data, op, alu_data);

endmodule

```


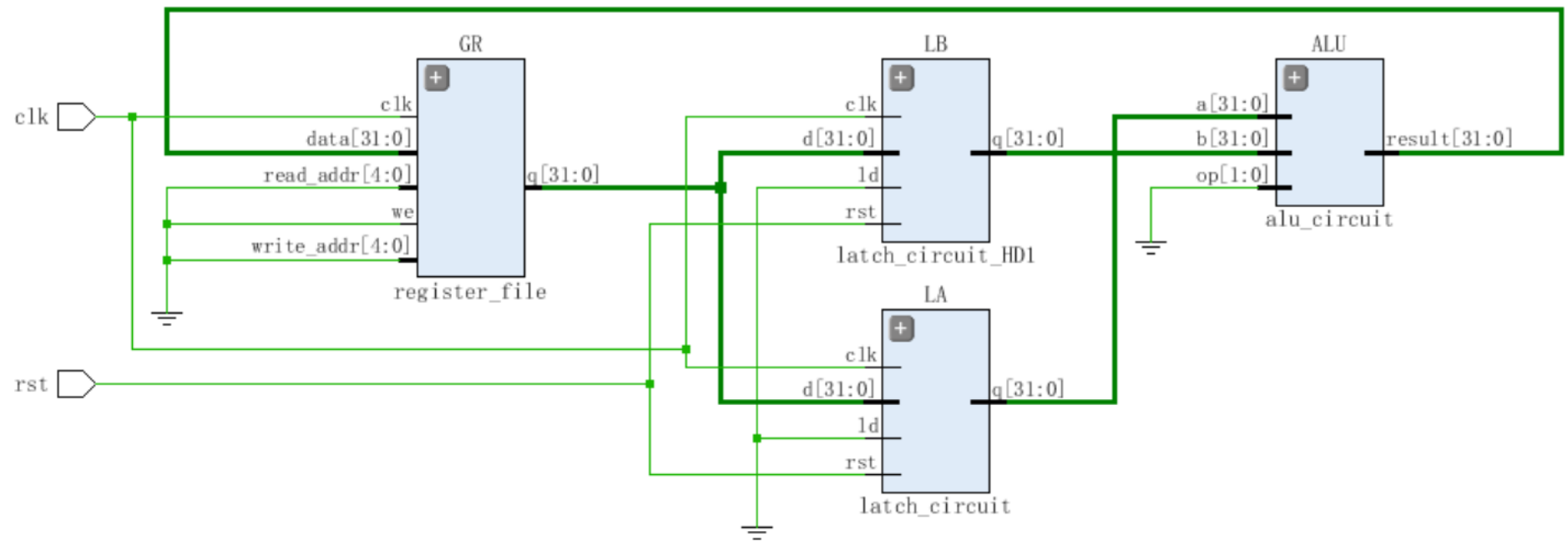


有限状态机FSM

Finite State Machine

Finite-State Machines (FSMs) and Controllers

 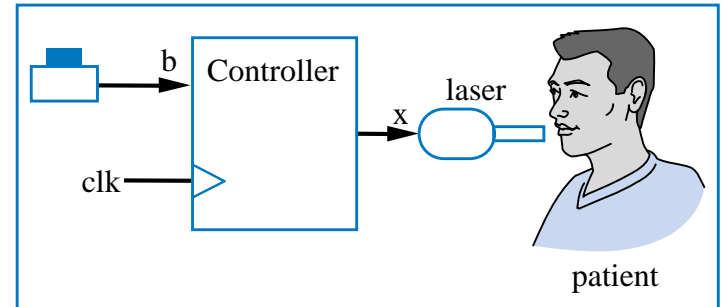- Want sequential circuit with particular behavior over time
- Example: Laser timer
 - Push button: $x=1$ for 3 clock cycles
 - How? Let's try three flip-flops
 - $b=1$ gets stored in first D flip-flop
 - Then 2nd flip-flop on next cycle, then 3rd flip-flop on next
 - OR the three flip-flop outputs, so x should be 1 for three cycles




Need a Better Way to Design Sequential Circuits

- Trial and error is not a good design method
 - Will we be able to “guess” a circuit that works for other desired behavior?
 - How about counting up from 1 to 9? Pulsing an output for 1 cycle every 10 cycles? Detecting the sequence 1 3 5 in binary on a 3-bit input?
 - And, a circuit built by guessing may have undesired behavior
 - Laser timer: What if press button again while $x=1$? x then stays one another 3 cycles. Is that what we want?
- Combinational circuit design process had two important things
 1. A formal way to describe desired circuit behavior
 - Boolean equation, or truth table
 2. A well-defined process to convert that behavior to a circuit
- We need those things for sequence circuit design

Describing Behavior of Sequential Circuit: FSM

- Finite-State Machine (FSM)



- A way to describe desired behavior of sequential circuit
 - Akin to Boolean equations for combinational behavior
- List states, and transitions among states
 - Example: Make x change toggle (0 to 1, or 1 to 0) every clock cycle
 - Two states: “Off” ($x=0$), and “On” ($x=1$)
 - Transition from Off to On, or On to Off, on rising clock edge
 - Arrow with no starting state points to initial state (when circuit first starts)

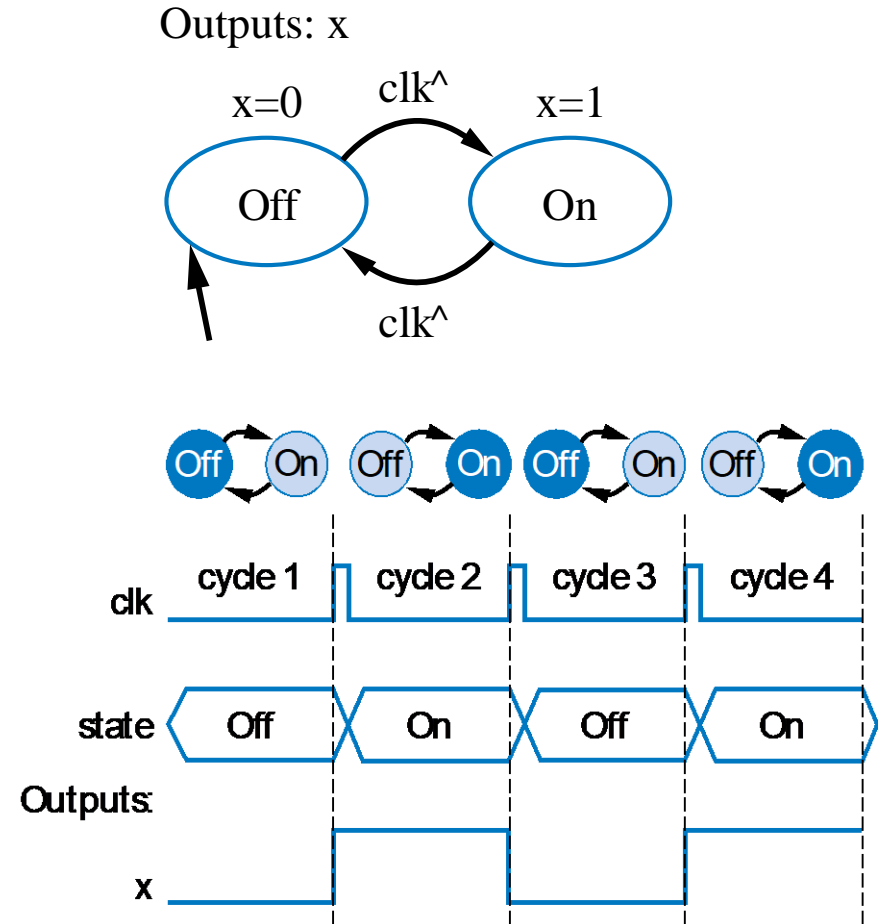

FSM Example: 0,1,1,1,repeat


- Want 0, 1, 1, 1, 0, 1, 1, 1, ...
 - Each value for one clock cycle
- Can describe as FSM
 - Four states
 - Transition on rising clock edge to next state

Outputs: x

  


Extend FSM to Three-Cycles High Laser Timer

 - Four states
- Wait in “Off” state while b is 0 (b')
- When b is 1 (and rising clock edge), transition to On1
 - Sets $x=1$
 - On next two clock edges, transition to On2, then On3, which also set $x=1$
- So $x=1$ for three cycles after button pressed



FSM Simplification: Rising Clock Edges Implicit

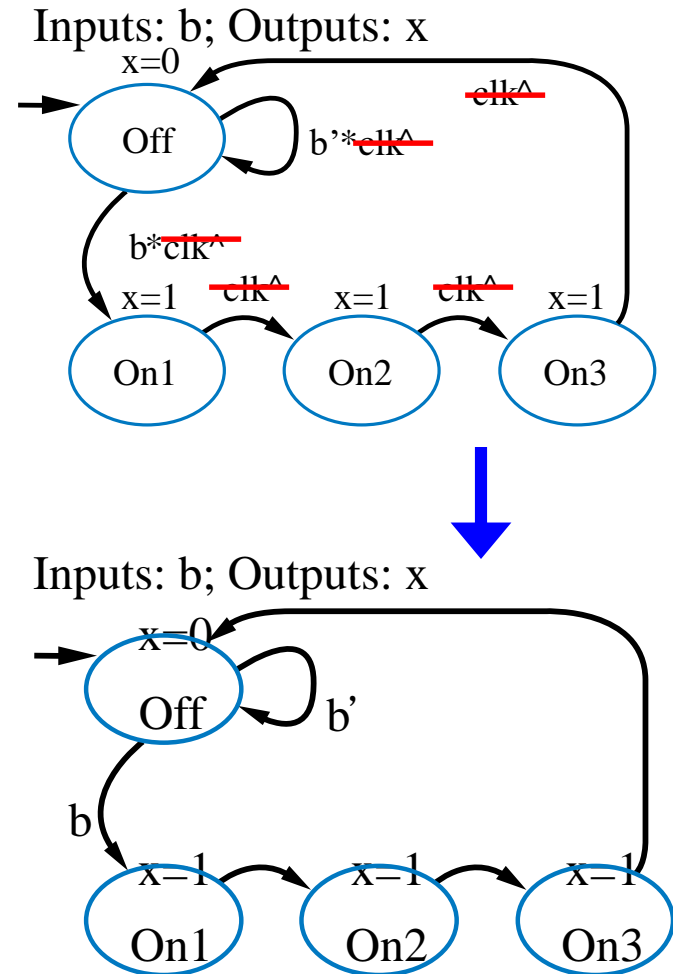
- Showing rising clock on every transition: cluttered
 - Make implicit -- assume every edge has rising clock, even if not shown
 - What if we wanted a transition *without* a rising edge
 - We don't consider such asynchronous FSMs -- less common, and advanced topic
 - Only consider **synchronous** FSMs -- rising edge on *every* transition



Note: Transition with no associated condition thus transitions to next state on next clock cycle

FSM Definition

 - FSM consists of
 - Set of states
 - Ex: {Off, On1, On2, On3}
 - Set of inputs, set of outputs
 - Ex: Inputs: {x}, Outputs: {b}
 - Initial state
 - Ex: “Off”
 - Set of transitions
 - Describes next states
 - Ex: Has 5 transitions
 - Set of actions
 - Sets outputs while in states
 - Ex: $x=0$, $x=1$, $x=1$, and $x=1$





We often draw FSM graphically, known as **state diagram**


Can also use table (state table), or textual languages

Standard Controller Architecture

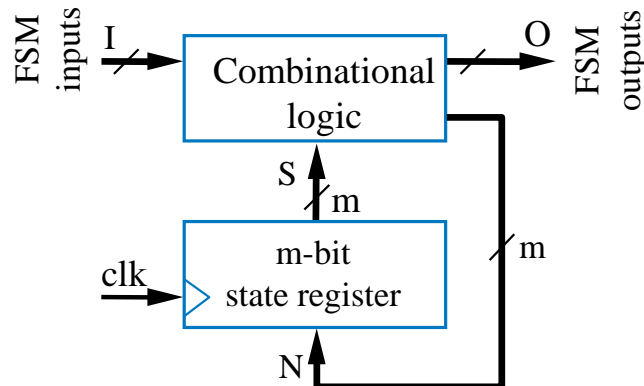 - How implement FSM as sequential circuit?
 - Use standard architecture
 - State register -- to store the present state
 - Combinational logic -- to compute outputs, and next state
 - For laser timer FSM
 - 2-bit state register, can represent four states
 - Input b, output x
 - Known as **controller**





General version

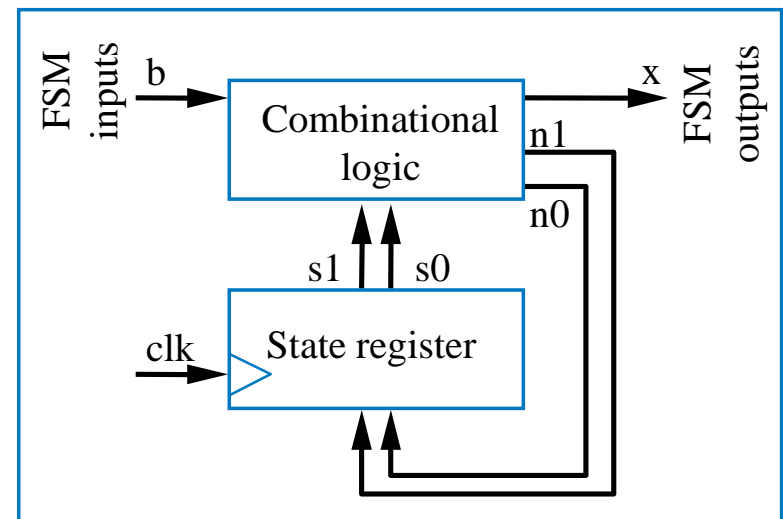

Finite-State Machines (FSMs)—Sequential Behavior

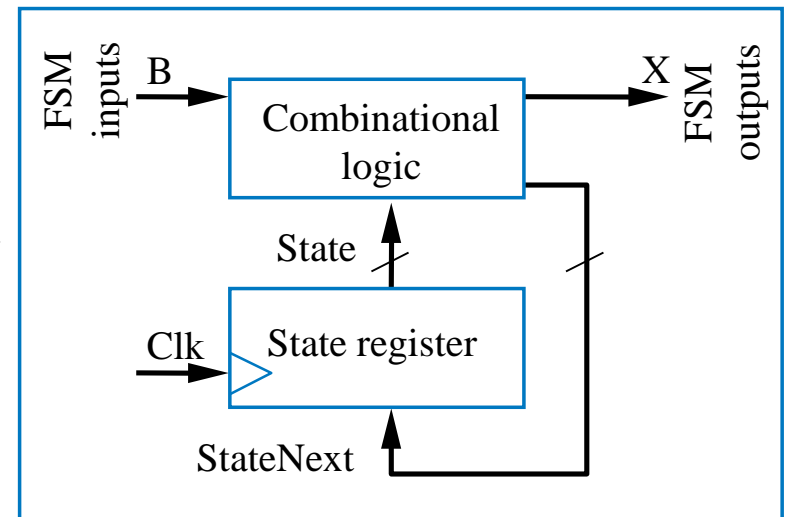 
- **Finite-state machine (FSM)** is a common model of sequential behavior
 - Example: If $B=1$, hold $X=1$ for 3 clock cycles
 - Note: Transitions implicitly ANDed with rising clock edge
 - Implementation model has two parts:
 - State register
 - Combinational logic
 - HDL model will reflect those two parts



Finite-State Machines (FSMs)—Sequential Behavior

Modules with Multiple Procedures and Shared Variables

Inputs: B; Outputs: X

 

```
`timescale 1 ns/1 ns
```

```
module LaserTimer(B, X, Clk, Rst);
```

```
    input B;
    output reg X;
    input Clk, Rst;
```

```
    parameter S_Off = 0, S_On1 = 1,
              S_On2 = 2, S_On3 = 3;
```

```
    reg [1:0] State, StateNext;
```

```
    // CombLogic
    always @(State, B) begin
        case (State)
            S_Off: begin
                X <= 0;
                if (B == 0)
                    StateNext <= S_Off;
                else
                    StateNext <= S_On1;
            end
            ...
        endcase
    end
```


```
    ...
    S_On1: begin
        X <= 1;
        StateNext <= S_On2;
    end
    S_On2: begin
        X <= 1;
        StateNext <= S_On3;
    end
    S_On3: begin
        X <= 1;
        StateNext <= S_Off;
    end
endcase
end

// StateReg
always @(posedge Clk) begin
    if (Rst == 1 )
        State <= S_Off;
    else
        State <= StateNext;
    end
endmodule
```

- Code will be explained on following slides

Finite-State Machines (FSMs)—Sequential Behavior

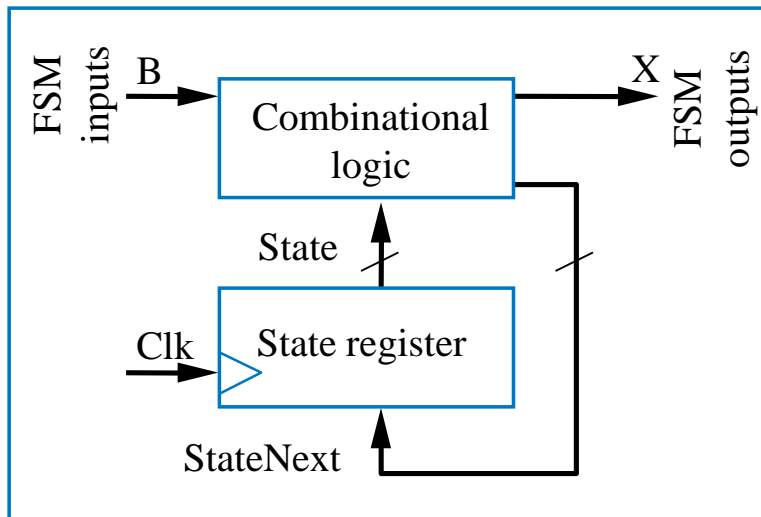- Modules has two procedures
 - One procedure for combinational logic
 - One procedure for state register
 - But it's still a behavioral description



```
`timescale 1 ns/1 ns

module LaserTimer(B, X, Clk, Rst);

    input B;
    output reg X;
    input Clk, Rst;

    parameter S_Off = 0, S_On1 = 1,
              S_On2 = 2, S_On3 = 3;

    reg [1:0] State, StateNext;

    // CombLogic
    always @(State, B) begin
        ...
    end

    // StateReg
    always @(posedge Clk) begin
        ...
    end
endmodule
```

Finite-State Machines (FSMs)—Sequential Behavior Parameters

- **parameter** declaration
 - Not a variable or net, but rather a *constant*
 - A constant is a value that must be initialized, and that cannot be changed within the module's definition
 - Four parameters defined
 - *S_Off*, *S_On1*, *S_On2*, *S_On3*
 - Correspond to FSM' s states
 - Should be initialized to unique values

```
`timescale 1 ns/1 ns

module LaserTimer(B, X, Clk, Rst);


    input B;
    output reg X;
    input Clk, Rst;

    parameter S_Off = 0, S_On1 = 1,
              S_On2 = 2, S_On3 = 3;

    reg [1:0] State, StateNext;


    // CombLogic
    always @(State, B) begin
        ...
    end

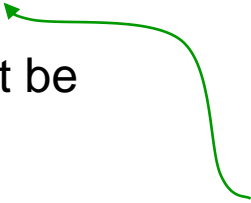    // StateReg
    always @(posedge Clk) begin
        ...
    end
endmodule
```



Finite-State Machines (FSMs)—Sequential Behavior

- Module declares two reg variables
 - *State*, *StateNext*
 - Each is 2-bit vector (need two bits to represent four unique state values 0 to 3)
 - Variables are shared between CombLogic and StateReg procedures
- CombLogic procedure
 - Event control sensitive to *State* and input *B*
 - Will output *StateNext* and *X*
- StateReg procedure
 - Sensitive to *Clk* input
 - Will output *State*, which it stores

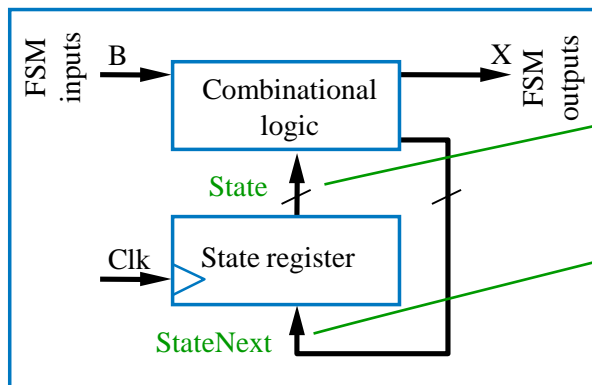

```
`timescale 1 ns/1 ns

module LaserTimer(B, X, Clk, Rst);

    input B;
    output reg X;
    input Clk, Rst;

    parameter S_Off = 0, S_On1 = 1,
              S_On2 = 2, S_On3 = 3;

    reg [1:0] State, StateNext;


    // CombLogic
    always @(State, B) begin
        ...
    end

    // StateReg
    always @(posedge Clk) begin
        ...
    end
endmodule
```

Finite-State Machines (FSMs)—Sequential Behavior Procedures with Case Statements


- Procedure may use **case** statement
 - Preferred over if-else-if when just one expression determines which statement to execute
 - **case** (expression)
 - Execute statement whose case item expression value matches case expression
 - *case item expression : statement*
 - *statement* is commonly a begin-end block, as in example
 - First case item expression that matches executes; remaining case items ignored
 - If no item matches, nothing executes
 - Last item may be "**default : statement**"
 - Statement executes if none of the previous items matched
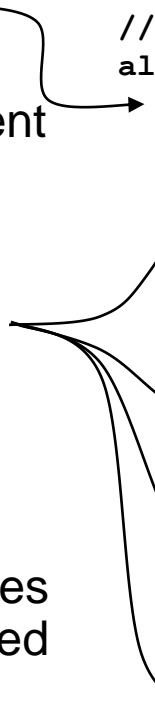
```
// CombLogic
always @(State, B) begin
  case (State)
    S_Off: begin
      X <= 0;
      if (B == 0)
        StateNext <= S_Off;
      else
        StateNext <= S_On1;
    end
    S_On1: begin
      X <= 1;
      StateNext <= S_On2;
    end
    S_On2: begin
      X <= 1;
      StateNext <= S_On3;
    end
    S_On3: begin
      X <= 1;
      StateNext <= S_Off;
    end
  endcase
end
```



Finite-State Machines (FSMs)—Sequential Behavior Procedures with Case Statements

 - FSM's CombLogic procedure
 - Case statement describes states
 - case (State)
 - Executes corresponding statement (often a begin-end block) based on State's current value
 - A state's statements consist of
 - Actions of the state
 - Setting of next state (transitions)
- Ex: State is S_On1
 - Executes statements for state On1, jumps to endcase



```

reg [1:0] State, StateNext;

// CombLogic
always @(State, B) begin
    case (State)
        S_Off: begin
            X <= 0;
            if (B == 0)
                StateNext <= S_Off;
            else
                StateNext <= S_On1;
            end
        S_On1: begin
            X <= 1;
            StateNext <= S_On2;
            end
        S_On2: begin
            X <= 1;
            StateNext <= S_On3;
            end
        S_On3: begin
            X <= 1;
            StateNext <= S_Off;
            end
    endcase
end
    
```

*Suppose State is
S_On1*

Finite-State Machines (FSMs)—Sequential Behavior

- FSM StateReg Procedure

- Similar to 4-bit register

- Register for State is 2-bit vector reg variable

```
...  
parameter S_Off = 0, S_On1 = 1,  
          S_On2 = 2, S_On3 = 3;
```

```
reg [1:0] State, StateNext;
```

- Procedure has synchronous reset


- Resets State to FSM' s initial state, S_Off

```
...  
// StateReg  
always @(posedge Clk) begin  
    if (Rst == 1 )  
        State <= S_Off;  
    else  
        State <= StateNext;  
end  
...
```

Finite-State Machines (FSMs)—Sequential Behavior

Modules with Multiple Procedures and Shared Variables

Inputs: B; Outputs: X

 

```
`timescale 1 ns/1 ns
```

```
module LaserTimer(B, X, Clk, Rst);
```

```
    input B;
    output reg X;
    input Clk, Rst;
```

```
    parameter S_Off = 0, S_On1 = 1,
              S_On2 = 2, S_On3 = 3;
```

```
    reg [1:0] State, StateNext;
```

```
    // CombLogic
    always @(State, B) begin
        case (State)
            S_Off: begin
                X <= 0;
                if (B == 0)
                    StateNext <= S_Off;
                else
                    StateNext <= S_On1;
            end
        endcase
    end
```

```
    ...
    S_On1: begin
        X <= 1;
        StateNext <= S_On2;
    end
    S_On2: begin
        X <= 1;
        StateNext <= S_On3;
    end
    S_On3: begin
        X <= 1;
        StateNext <= S_Off;
    end
endcase
end


// StateReg
always @(posedge Clk) begin
    if (Rst == 1 )
        State <= S_Off;
    else
        State <= StateNext;
    end
endmodule
```

- Code should now be clear

Finite-State Machines (FSMs)—Sequential Behavior

Self-Checking Testbenches

 - FSM testbench
 - First part of file (variable/net declarations, module instantiations) similar to before
 - Vector Procedure
 - Resets FSM
 - Sets FSM's input values (“test vectors”)
 - Waits for specific clock cycles
 - We observe the resulting waveforms to determine if FSM behaves correctly



```


...
// Clock Procedure
always begin
    Clk_s <= 0;
    #10;
    Clk_s <= 1;
    #10;
end // Note: Procedure repeats

// Vector Procedure
initial begin
    Rst_s <= 1;
    B_s <= 0;
    @(posedge Clk_s);
    #5 Rst_s <= 0;
    @(posedge Clk_s);
    #5 B_s <= 1;
    @(posedge Clk_s);
    #5 B_s <= 0;
    @(posedge Clk_s);
    @(posedge Clk_s);
    @(posedge Clk_s);
end
endmodule
    
```

Finite-State Machines (FSMs)—Sequential Behavior

Self-Checking Testbenches

 - Reading waveforms is error-prone
- Create *self-checking testbench*
 - Use *if* statements to check for expected values
 - If a check fails, print error message
 - Ex: if X_s fell to 0 one cycle too early, simulation might output:
 - 95: Third X=1 failed



```
// Vector Procedure
initial begin
    Rst_s <= 1;
    B_s <= 0;
    @(posedge Clk_s);
    #5 if (X_s != 0)
        $display("%t: Reset failed", $time);
    Rst_s <= 0;
    @(posedge Clk_s);
    #5 B_s <= 1;
    @(posedge Clk_s);
    #5 B_s <= 0;
    if (X_s != 1)
        $display("%t: First X=1 failed", $time);
    @(posedge Clk_s);
    #5 if (X_s != 1)
        $display("%t: Second X=1 failed", $time);
    @(posedge Clk_s);
    #5 if (X_s != 1)
        $display("%t: Third X=1 failed", $time);
    @(posedge Clk_s);
    #5 if (X_s != 0)
        $display("%t: Final X=0 failed", $time);
end
```



Finite-State Machines (FSMs)—Sequential Behavior

\$display System Procedure

- **\$display** – built-in Verilog system procedure for printing information to display during simulation
 - A **system procedure** interacts with the simulator and/or host computer system
 - To write to a display, read a file, get the current simulation time, etc.
 - Starts with **\$** to distinguish from regular procedures
- String argument is printed literally...
 - `$display("Hello")` will print "Hello"
 - Automatically adds newline character
- ...except when special sequences appear
 - **%t**: Display a time expression
 - Time expression must be next argument
 - **\$time** – Built-in system procedure that returns the current simulation time
 - *95: Third X=1 failed* ←


```
// Vector Procedure
initial begin
    Rst_s <= 1;
    B_s <= 0;
    @(posedge Clk_s);
    #5 if (X_s != 0)
        $display("%t: Reset failed", $time);
    Rst_s <= 0;
    @(posedge Clk_s);
    #5 B_s <= 1;
    @(posedge Clk_s);
    #5 B_s <= 0;
    if (X_s != 1)
        $display("%t: First X=1 failed", $time);
    @(posedge Clk_s);
    #5 if (X_s != 1)
        $display("%t: Second X=1 failed", $time);
    @(posedge Clk_s);
    #5 if (X_s != 1)
        $display("%t: Third X=1 failed", $time);
    @(posedge Clk_s);
    #5 if (X_s != 0)
        $display("%t: Final X=0 failed", $time);
end
```

  Controller Example: Button Press Synchronizer




- Want simple sequential circuit that converts button press to single cycle duration, regardless of length of time that button actually pressed
 - We assumed such an ideal button press signal in earlier example, like the button in the laser timer controller

 Controller Example: Button Press Synchronizer (cont)




Step 1: FSM

 


Step 3: Encode states

	Combinational logic Inputs			Outputs		
	s1	s0	bi	n1	n0	bo
A	0	0	0	0	0	0
	0	0	1	0	1	0
B	0	1	0	0	0	1
	0	1	1	1	0	1
C	1	0	0	0	0	0
	1	0	1	1	0	0
unused	1	1	0	0	0	0
	1	1	1	0	0	0

Step 4: State table

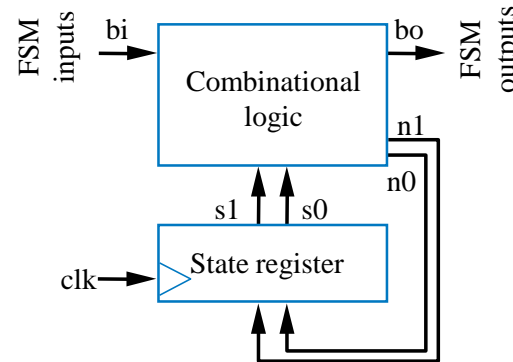

Step 2: Create architecture



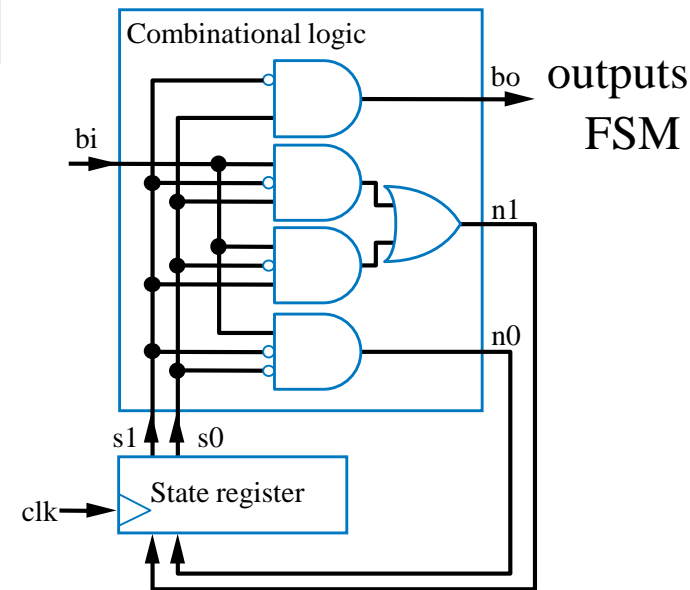


Step 5: Create combinational circuit

Step 5: Create combinational circuit

Controller Example: Sequence Generator

 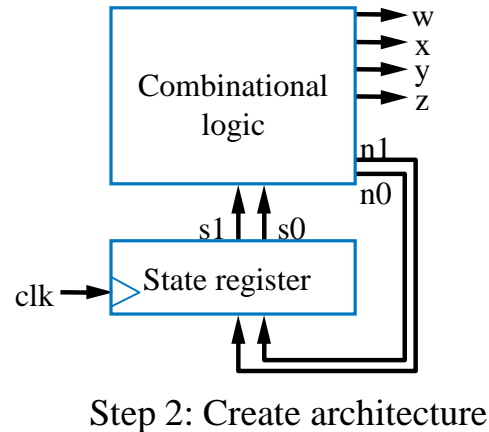 
- Want generate sequence 0001, 0011, 1100, 1000, (repeat)
 - Each value for one clock cycle
 - Common, e.g., to create pattern in 4 lights, or control magnets of a “stepper motor”



Inputs		Outputs					
s1	s0	w	x	y	z	n1	n0
A	0	0	0	0	1	0	1
B	0	0	0	1	1	1	0
C	1	1	1	0	0	1	1
D	1	1	0	0	0	0	0


Step 4: Create state table
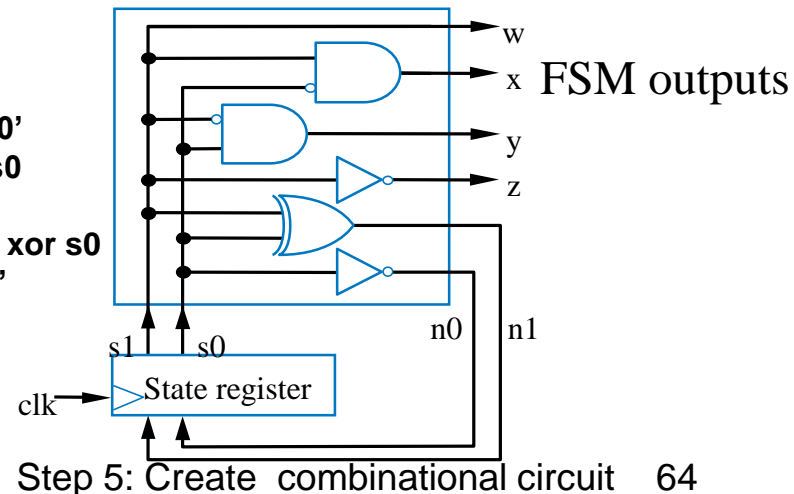
$$\begin{aligned}
 w &= s1 \\
 x &= s1s0' \\
 y &= s1's0 \\
 z &= s1' \\
 n1 &= s1 \text{ xor } s0 \\
 n0 &= s0'
 \end{aligned}$$




Initial State of a Controller

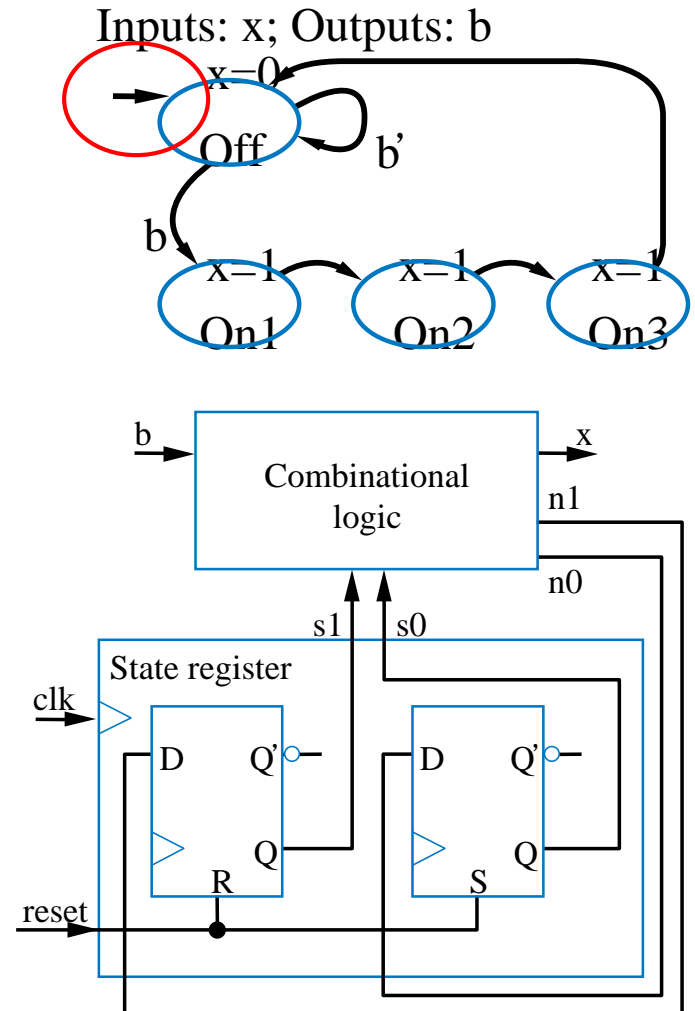- All our FSMs had initial state
 - But our sequential circuit designs did not
 - Can accomplish using flip-flops with reset/set inputs
 - Shown circuit initializes flip-flops to 01
 - Designer must ensure reset input is 1 during power up of circuit
 - By electronic circuit design




Describing Safe FSMs

- **Safe FSM** – If enters illegal state, transitions to a legal state
- **Example**
 - Suppose example has only three states
 - Two-bit encoding has illegal state encoding "11"
 - Also known as "unreachable" state
 - Not possible to enter that state under normal FSM operation
 - But actually possible to enter that state due to circuit error – e.g., electrical noise that causes state register bit to switch

 

Describing Safe FSMs

 - **Safe FSM** – If enters illegal state, transitions to a legal state
- **Example**
 - Suppose example has only three states
 - Two-bit encoding has illegal state encoding "11"
 - Safe implementation
 - Transition to appropriate legal state
 - Even though that undefined state appears to be unreachable
 - Thus, FSM recovers from the error



Describing Safe FSMs in Verilog HDL

- Unsafe FSM description
 - Only describes legal states, ignores illegal states
- Some synthesis tools support "safe" option during synthesis
 - Automatically creates safe FSM from an unsafe FSM description

```
...  
    reg [1:0] State, StateNext;  
  
    always @(State, B) begin  
        case (State)  
            S_Off: begin  
                X <= 0;  
                if (B == 0)  
                    StateNext <= S_Off;  
                else  
                    StateNext <= S_On1;  
            end  
            S_On1: begin  
                X <= 1;  
                StateNext <= S_On2;  
            end  
            S_On2: begin  
                X <= 1;  
                StateNext <= S_Off;  
            end  
        endcase  
    end  
...
```

Describing Safe FSMs in Verilog HDL


- Explicitly describing a safe FSM
 - Include case item(s) to describe illegal states
 - Can use "default" case item
 - Executes if State equals anything other than S_Off, S_On1, or S_On2
- Note: Use of *default* is wise regardless of number of states
 - Even if number is power of two, because state encoding may use more than minimum number of bits
 - e.g., one-hot encoding has many more illegal states than legal states
- Note: If synthesis tool support "safe" option, *use it*
 - Otherwise, tool may automatically optimize away unreachable states to improve performance and size, but making state machine unsafe

```
...  
    reg [1:0] State, StateNext;  
  
    always @(State, B) begin  
        case (State)  
            S_Off: begin  
                X <= 0;  
                if (B == 0)  
                    StateNext <= S_Off;  
                else  
                    StateNext <= S_On1;  
            end  
            S_On1: begin  
                X <= 1;  
                StateNext <= S_On2;  
            end  
            S_On2: begin  
                X <= 1;  
                StateNext <= S_Off;  
            end  
            default: begin  
                X <= 0;  
                StateNext <= S_Off;  
            end  
        endcase  
    end  
...
```

Verilog设计深入


双向端口设计

```
module bi4b(TRI_PORT, DOUT, DIN, ENA, CTRL);  
    inout TRI_PORT;  
    input DIN, ENA, CTRL;  
    output DOUT;  
  
    assign TRI_PORT = ENA ? DIN : 1'bz;  
    assign DOUT = TRI_PORT | CTRL;  
  
endmodule
```

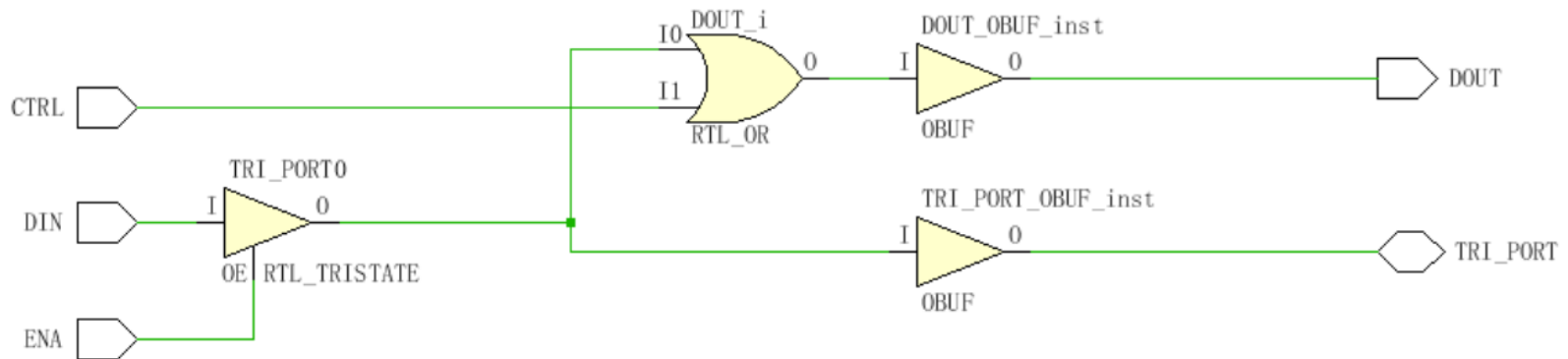

Resets

- **Reset** – Behavior of a register when a reset input is asserted
- Good practice dictates having defined reset behavior for every register
- Reset behavior should always have priority over normal register behavior
- Reset behavior
 - Usually clears register to 0s
 - May initialize to other value
 - e.g., state register of a controller may be initialized to encoding of initial state of FSM
- Reset usually asserted externally at start of sequential circuit operation, but also to restart due to failure, user request, or other reason

 

```
`timescale 1 ns/1 ns


module Reg4(I, Q, Clk, Rst);

    input [3:0] I;
    output [3:0] Q;
    reg [3:0] Q;
    input Clk, Rst;


    always @(posedge Clk) begin
        if (Rst == 1 )
            Q <= 4'b0000;
        else
            Q <= I;
        end
    endmodule
```


Synchronous Reset

 - Previous examples used **synchronous resets**
 - Rst** input only considered during rising clock



Rst=1 has no effect until rising clock

 

```
`timescale 1 ns/1 ns
```

```
module Reg4(I, Q, Clk, Rst);
```

```
    input [3:0] I;
    output [3:0] Q;
    reg [3:0] Q;
    input Clk, Rst;
```


```
    always @(posedge Clk) begin
        if (Rst == 1 )
            Q <= 4'b0000;
        else
            Q <= I;
        end
    endmodule
```

Asynchronous Reset


- Can also use **asynchronous reset**

– **Rst** input considered independently from clock


- Add "posedge Rst" to sensitivity list

 

Asynchronous reset

 

Synchronous reset

 

```
`timescale 1 ns/1 ns

module Reg4(I, Q, Clk, Rst);
```

```
    input [3:0] I;
    output [3:0] Q;
    reg [3:0] Q;
    input Clk, Rst;
```

```
always @(posedge Clk, posedge Rst) begin
    if (Rst == 1)
        Q <= 4'b0000;
    else
        Q <= I;
    end
endmodule
```

Asynchronous Reset

- Could have used asynchronous reset for FSM state register too

```
...  
// StateReg  
always @(posedge Clk) begin  
    if (Rst == 1 )  
        State <= S_Off;  
    else  
        State <= StateNext;  
    end  
...
```

Synchronous

```
...  
// StateReg  
always @(posedge Clk, posedge Rst) begin  
    if (Rst == 1 )  
        State <= S_Off;  
    else  
        State <= StateNext;  
    end  
...
```





Asynchronous

Synchronous versus Asynchronous Resets

- Which is better – synchronous or asynchronous reset?
 - Hotly debated in design community
 - Each has pros and cons
 - e.g., asynchronous can still reset even if clock is not functioning, synchronous avoids timing analysis problems sometimes accompanying asynchronous designs
 - We won't try to settle the debate here
 - What's important is to be *consistent* throughout a design
 - All registers should have defined reset behavior that takes priority over normal register behavior
 - That behavior should all be synchronous reset or all be asynchronous reset
 - We will use synchronous resets in all of our remaining examples

Non-Ideal Flip-Flop Behavior

  
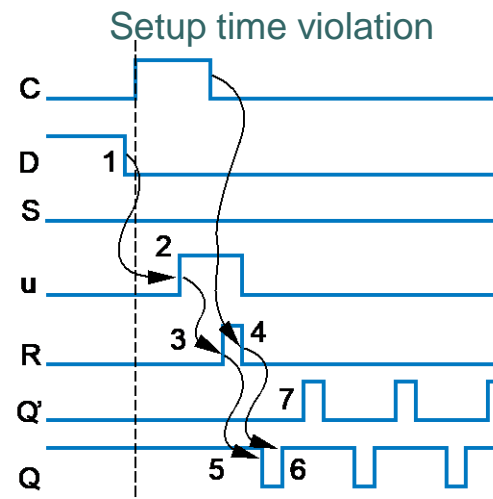
 
- Can't change flip-flop input too close to clock edge
 - Setup time: time that D must be stable *before* edge
 - ⑩ Else, stable value not present at internal latch
 - Hold time: time that D must be held stable *after* edge
 - ⑩ Else, new value doesn't have time to loop around and stabilize in internal latch



Leads to oscillation!

Metastability


- Violating setup/hold time can lead to bad situation known as **metastable** state
 - Metastable state: Any flip-flop state other than stable 1 or 0
 - ⑩ Eventually settles to one or other, but we don't know which
 - For internal circuits, we can make sure observe setup time
 - But what if input comes from external (asynchronous) source, e.g., button press?
- Partial solution
 - Insert synchronizer flip-flop for asynchronous input
 - ⑩ Special flip-flop with very small setup/hold time
 - Doesn't completely prevent metastability

   

Metastability

- One flip-flop doesn't completely solve problem
- How about adding more synchronizer flip-flops?
 - Helps, but just decreases probability of metastability
- So how solve completely?
 - Can't! May be unsettling to new designers. But we just can't guarantee a design that won't ever be metastable. We can just minimize the mean time between failure (MTBF) -- a number often given along with a circuit

 Probability of flip-flop being metastable is...



■ 资源优化之资源共享

【例 9-1】

```
module multmux (A0, A1, B, S, R);  
  input[3:0] A0, A1, B;  input S;  
  output[7:0] R;  reg[7:0] R;  
  always @(A0 or A1 or B or S)  
  begin  
    if (S==1'b0) R<=A0 * B;  
    else R<=A1 * B ;  end  
endmodule
```

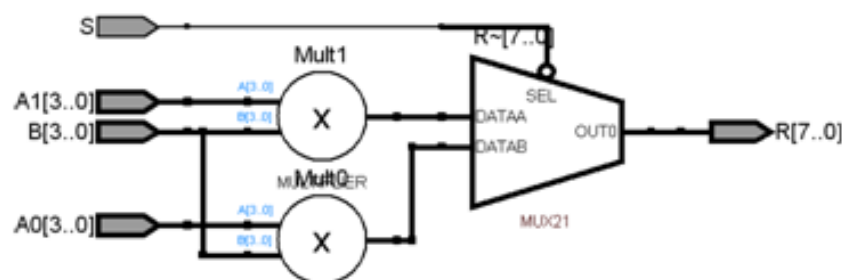


图 9-1 先乘后选择的设计方法 RTL 结构

【例 9-2】

```
module multmux (A0, A1, B, S,R);  
  input[3:0] A0, A1, B;  input S;  
  output[7:0] R;  wire [7:0] R;  
  reg [3:0] TEMP;  
  always @(A0 or A1 or B or S)  
  begin if (S==1'b0) TEMP<=A0;  
    else TEMP <= A1;  end  
  assign R=TEMP * B;  
endmodule
```

 


图 9-2 先选择后乘设计方法 RTL 结构

■ 资源优化之逻辑优化

【例 9-3】

```
module mult1 (clk, ma, mc);  
  input clk;  input[11:0] ma;  
  output[23:0] mc;  
  reg[23:0] mc; reg[11:0] ta,tb;  
  always @(posedge clk)  
  begin  ta<=ma; mc<=ta * tb;  
        tb <= 12'b100110111001; end  
endmodule
```

【例 9-4】

```
module mult2 (clk, ma, mc);  
  input clk;  input[11:0] ma;  
  output[23:0] mc;  
  reg[23:0] mc;  reg[11:0] ta;  
  parameter tb=12'b100110111001;  
  always @(posedge clk)  
  begin  ta<=ma ; mc<=ta * tb; end  
endmodule
```

■ 速度优化之流水线技术



图 9-4 未使用流水线

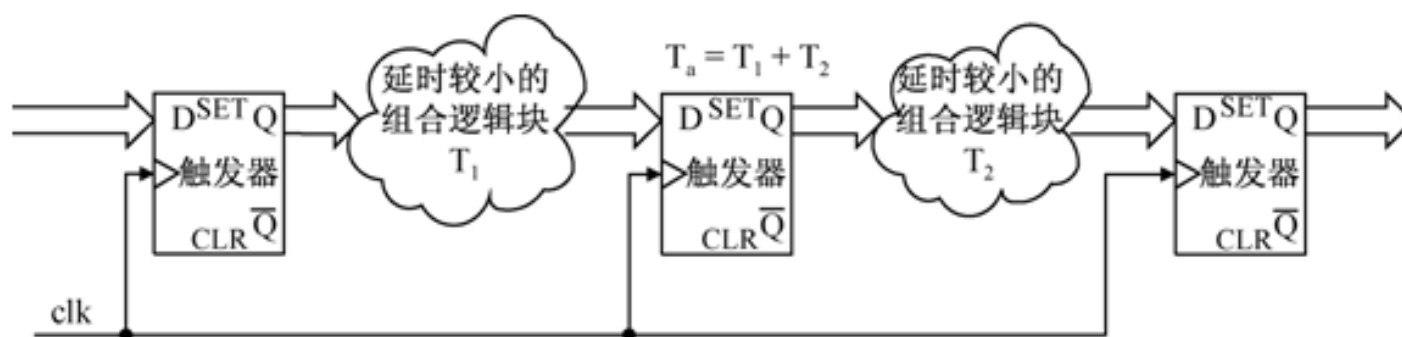


图 9-5 使用流水线结构

■ 速度优化之乒乓操作

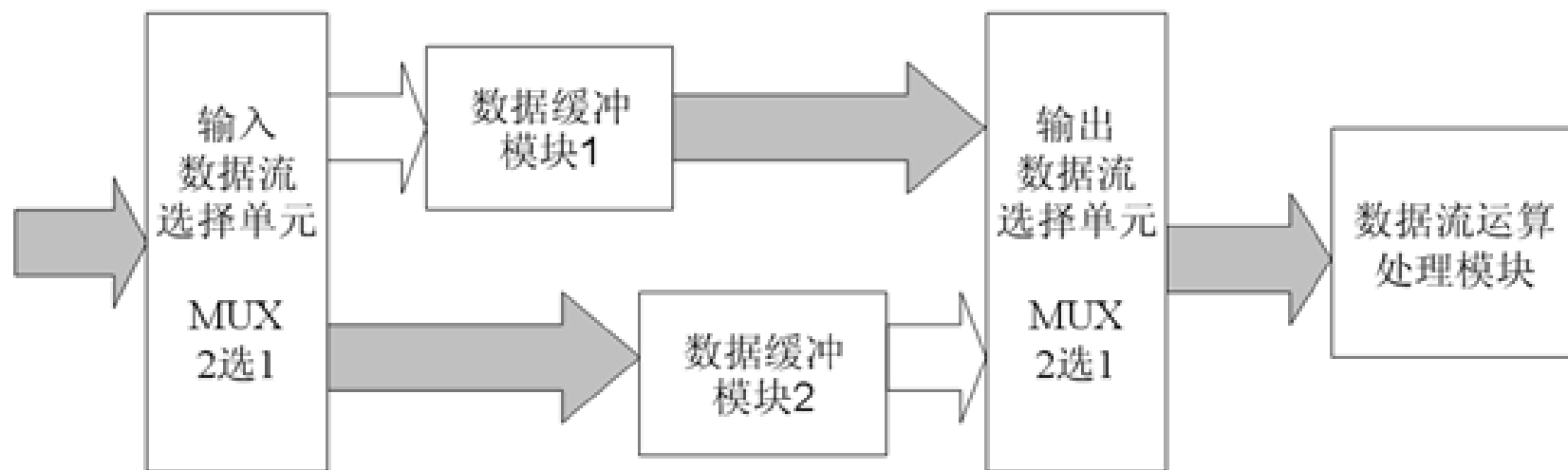


图 9-13 乒乓操作数据缓存结构示意图